

Digital System Design

Module 5 - COUNTERS AND SHIFT REGISTERS

Dr. Deepthi Sasidharan


Assistant Professor, Department of Information Technology
GEC Barton Hill, Thiruvananthapuram

November 17, 2020


Counters and Registers

- ▶ A clocked sequential circuit consists of a group of flip-flops and combinational gates.
- ▶ A circuit with flip-flops is considered a sequential circuit even in the absence of combinational gates.
- ▶ Circuits that include flip-flops are usually classified by the function they perform rather than by the name of the sequential circuit.
 - ▶ A **register** is a group of flip-flops, each one of which shares a common clock and is capable of storing one bit of information.
 - ▶ A **counter** is essentially a register that goes through a predetermined sequence of binary states.

4-bit register

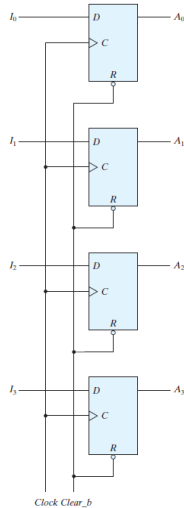

4-bit register with parallel load

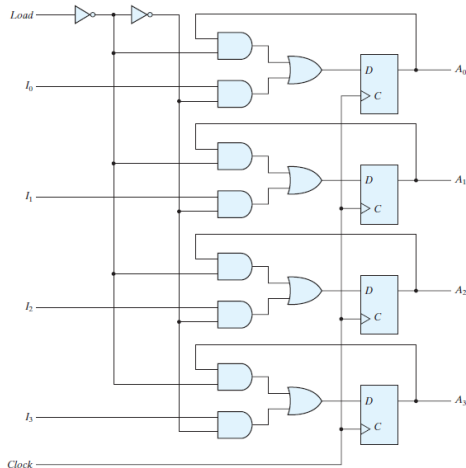

4-bit shift register

