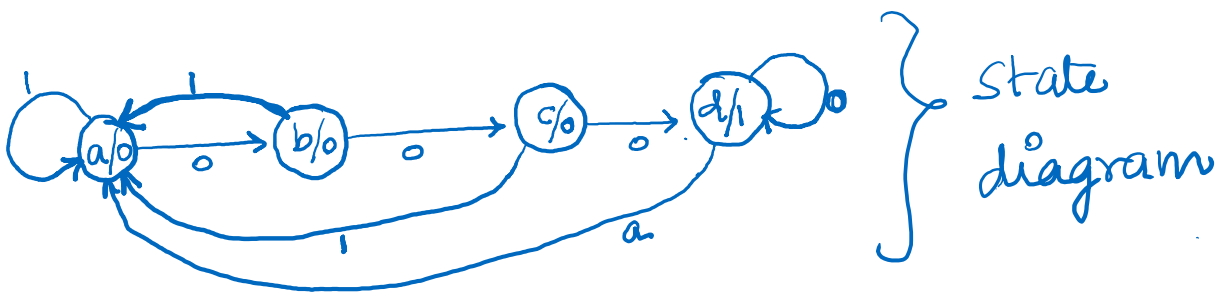


- ▶ From the word description and specifications of the desired operation, derive a state diagram for the circuit.
- ▶ Reduce the number of states if necessary.
- ▶ Assign binary values to the states.
- ▶ Obtain the binary-coded state table.
- ▶ Choose the type of flip-flops to be used.
- ▶ Derive the simplified flip-flop input equations and output equations.
- ▶ Draw the logic diagram.

Design a circuit that detects a sequence of 3 or more consecutive zeros



Binary assignment to the state

$a = \underline{00}$	$b = \underline{01}$	$c = \underline{10}$	$d = \underline{11}$
----------------------	----------------------	----------------------	----------------------

Binary coded state table.

	Present state		input	next state		output
	A	B	x	A(t+1)	B(t+1)	y
a)	0	0	0	0	<u>1</u>	0
	0	0	1	0	0	0
b)	0	1	0	<u>1</u>	0	0
	0	1	1	0	0	0
c)	1	0	0	<u>1</u>	<u>1</u>	0
	1	0	1	0	0	0
d)	1	1	0	<u>1</u>	<u>1</u>	1
	1	1	1	0	0	1

choose a flip flop to implement the circuit
available choices are D, JK, T flip flops



D Flip Flop to implement the circuit
characteristic equation of D Flip Flop.

$$Q(t+1) = D$$

$$A(t+1) = D_A = A\bar{x} + B\bar{x}$$

$$B(t+1) = D_B = A\bar{x} + \bar{B}\bar{x}$$

$$y = AB$$

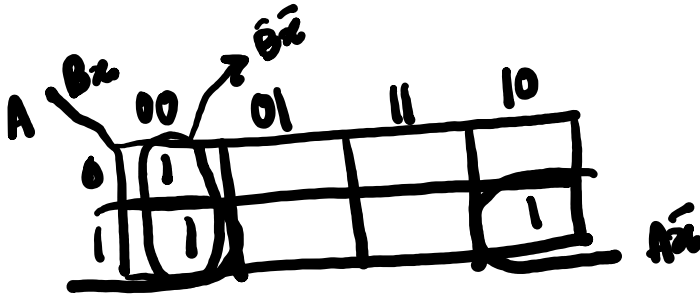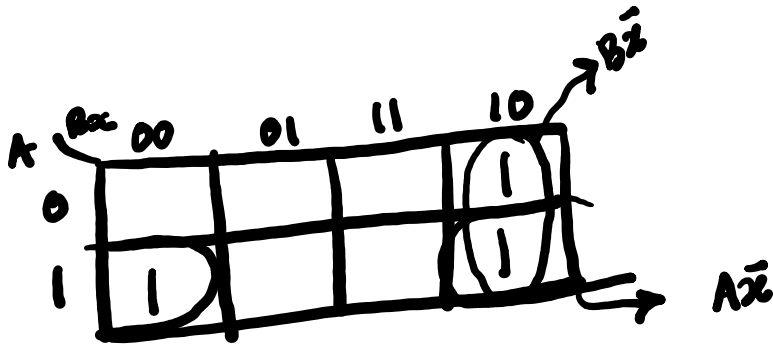

$$\underline{A(t+1) = A\bar{x} + B\bar{x}}$$

$$\underline{B(t+1) = A\bar{x} + \bar{B}\bar{x}}$$

$$y = AB.$$

