



**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**

**LOGIC SYSTEM DESIGN (CST-203)**

**MODULE 4**  
**NOTES**

PREPARED BY : JIBIN EP, ASSISTANT PROFESSOR, EKC TC MANJERI

# INDEX

SL No	Topic	Slide Link	Video Link
1	INTRODUCTION TO SEQUENTIAL CIRCUITS	<a href="#"><u>INTRODUCTION TO SEQUENTIAL CIRCUITS</u></a>	<a href="https://youtu.be/9NitpW-Rmzs"><u>https://youtu.be/9NitpW-Rmzs</u></a>
2	SR LATCH LATCH VS FLIPFLOP	<a href="#"><u>SR LATCH LATCH VS FLIPFLOP</u></a>	<a href="https://youtu.be/y8NewzE4DqA"><u>https://youtu.be/y8NewzE4DqA</u></a>
3	SR FLIPFLOP	<a href="#"><u>SR FLIPFLOP</u></a>	<a href="https://youtu.be/23C2FGN_wts"><u>https://youtu.be/23C2FGN_wts</u></a>
4	D FLIPFLOP	<a href="#"><u>D FLIPFLOP</u></a>	<a href="https://youtu.be/tyV1RLUSsAM"><u>https://youtu.be/tyV1RLUSsAM</u></a>
5	JK FLIPFLOP	<a href="#"><u>JK FLIPFLOP</u></a>	<a href="https://youtu.be/zuH42Y7dH3M"><u>https://youtu.be/zuH42Y7dH3M</u></a>
6	T FLIPFLOP	<a href="#"><u>T FLIPFLOP</u></a>	<a href="https://youtu.be/zuH42Y7dH3M"><u>https://youtu.be/zuH42Y7dH3M</u></a>

YOUTUBE : SHASTRA TECHNICAL INSTITUTE

# INDEX

SL No	Topic	Slide Link	Video Link
7	RACE AROUND CONDITION AND MASTER SLAVE JK FLIPFLOP	<a href="#">RACE AROUND CONDITION AND MASTER SLAVE JK FLIPFLOP</a>	<a href="https://youtu.be/cRjDzE11Pk4">https://youtu.be/cRjDzE11Pk4</a>
8	TRUTH TABLE , CHARACTERISTIC TABLE, EXCITATION TABLE CHARACTERISTIC EQUATION OF FLIPFLOP	<a href="#">TRUTH TABLE , CHARACTERISTIC TABLE, EXCITATION TABLE CHAR...</a>	<a href="https://youtu.be/nDnfLDjOxv0">https://youtu.be/nDnfLDjOxv0</a>
9	INTRODUCTION TO COUNTERS	<a href="#">INTRODUCTION TO COUNTERS</a>	<a href="https://youtu.be/LP48440m570">https://youtu.be/LP48440m570</a>
10	ASYNCHRONOUS UP AND DOWN COUNTER	<a href="#">ASYNCHRONOUS UP AND DOWN COUNTER</a>	<a href="https://youtu.be/LP48440m570">https://youtu.be/LP48440m570</a>
11	MODULO COUNTER	<a href="#">MODULO COUNTER</a>	<a href="https://youtu.be/LP48440m570">https://youtu.be/LP48440m570</a>
12	SYNCHONOUS COUNTER	<a href="#">SYNCHONOUS COUNTER</a>	<a href="https://youtu.be/PF39iLI1r4g">1https://youtu.be/PF39iLI1r4g</a> <a href="https://youtu.be/PF39iLI1r4g">https://youtu.be/PF39iLI1r4g</a>

## Module IV

### Sequential logic circuits:

Flip-flops- SR, JK, T and D. Triggering of flip-flops- Master slave flip-flops, Edge-triggered flip-flops. Excitation table and characteristic equation. Registers- register with parallel load. Counter design: Asynchronous counters- Binary and BCD counters, timing sequences and state diagrams. Synchronous counters- Binary Up-down counter, BCD counter.

YOUTUBE : SHASTRA TECHNICAL INSTITUTE

## MODULE 4 (TOPIC-1)

# INTRODUCTION TO SEQUENTIAL CIRCUITS

<https://youtu.be/9NitpW-Rmz>




YOUTUBE : SHASTRA TECHNICAL INSTITUTE

# SEQUENTIAL CIRCUIT

- Sequential Circuit is a combinational circuit with Memory
- The output of Sequential Circuit depends upon the **Present Input** and **Past Output [ Present State ]**
- The Information stored in the circuit represent Preset State
- The Present State and Present Input Will define the Output and Next State

In Sequential Circuit the Present Output depends on Present Input as well as Past Output / Past Outputs

# SEQUENTIAL LOGIC CIRCUIT

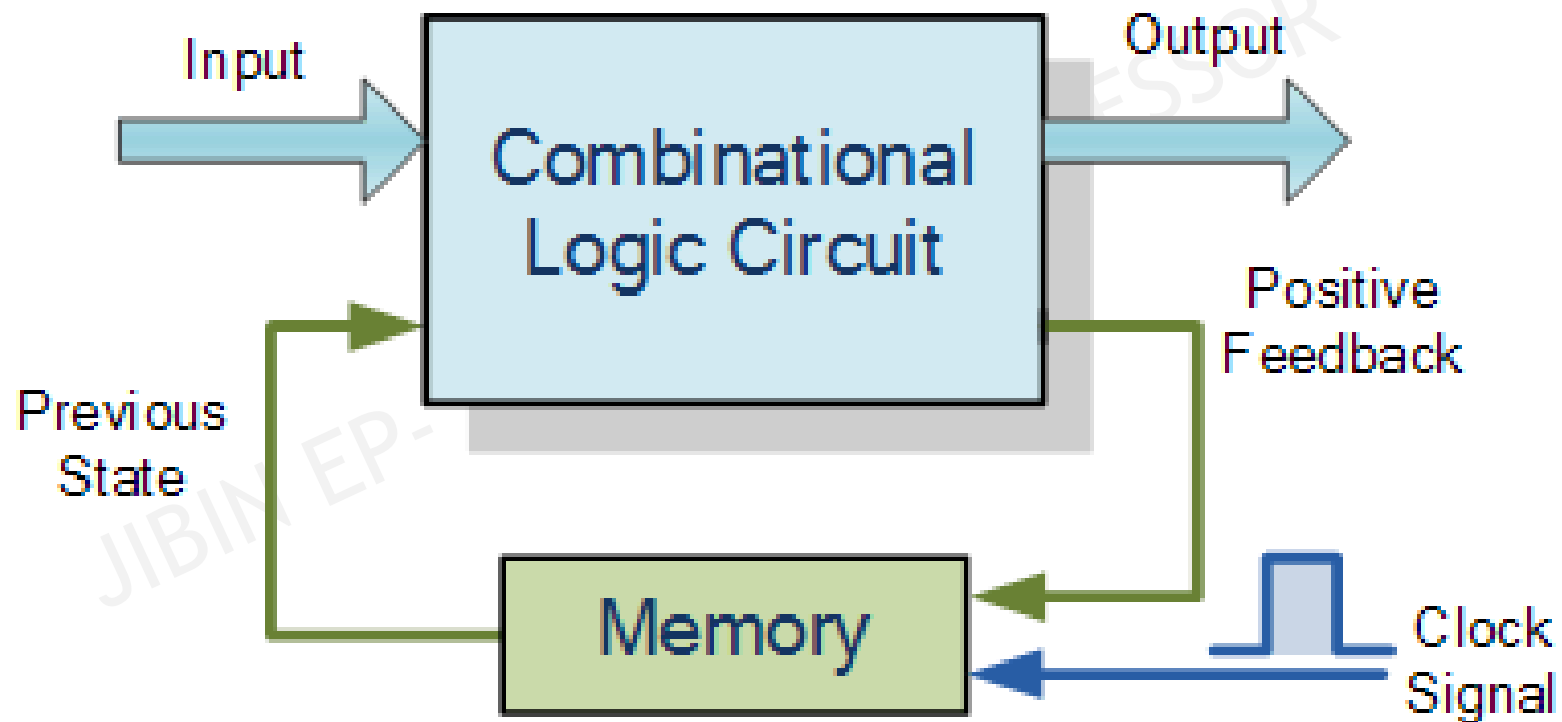

# Combinational Circuit

Output is Only depends on the Present Input

Memory Element is Absent

No Clock Signal is Applied




Example : Half Adder , Full Adder, Multiplexer

# Sequential Circuit

Output depends on Present input and Past Output

Presence of Memory Element

Clock signal is Required

 

Examples : Flpflip , Counters and Registers



# TYPES OF SEQUENTIAL CIRCUIT



Flipflop






Counter



Shift Register

# TRIGGERING METHODS

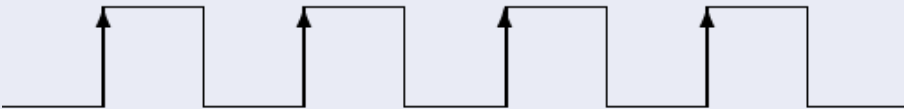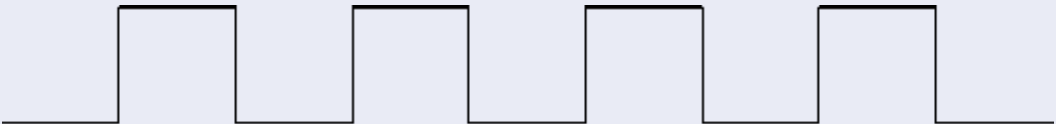
Edge Triggering	Level Triggering
Types of triggering that allows a circuit to become active at positive edge or negative edge of the clock signal	Types of triggering that allows a circuit to become active when the clock pulse is on a particular level
An Event occurs at the rising edge or falling edge	An Event occurs during the high voltage level or low voltage level
Flipflops are edge triggered	Latches are level triggered
	

 

(a) Level trigger.



(b) Positive-edge trigger.

 

(c) Negative-edge trigger.

Time  $\longrightarrow$

# TYPES OF FLIPFLOPS



SR FLIPFLOP

D FLIPFLOP

JK FLIPFLOP

T FLIPFLOP

MASTER SLAVE JK FLIPFLOP

## MODULE 4 (TOPIC-2)

# SR LATCH LATCH VS FLIPFLOP

<https://youtu.be/y8NewzE4DqA>

YOUTUBE : SHASTRA TECHNICAL INSTITUTE



## Latch

## Flipflop

Building block of sequential circuit,  
Built using Logic Gates

Building block of sequential circuit,  
built using Latches

Check input continuously and Changes  
output correspondingly

Check the input continuously and check  
the output in a continuous manner only  
with clock signal

Work with only binary inputs

Work with binary input and clock signal

Can not used as register


Can be used as a register

No Clock Signal

FF has clock signal

# SR LATCH


A	B	A <b>NAND</b> B
0	0	1
0	1	1
1	0	1
1	1	0

 

Active Low SR Latch can be constructed using two cross coupled NAND Gate

Suppose initially,  $Q = 1$  and  $\bar{Q} = 0$ . If inputs are  $S = 0$  and  $R = 0$ ,  $G_1$  inputs are a 0 ( $S$ ) and a 0 ( $\bar{Q}$ ). So, its output  $Q = 1$ .  $G_2$  inputs are a 0 ( $R$ ) and a 1 ( $Q$ ) and so its output  $\bar{Q} = 1$ . Now, suppose  $Q = 0$  and  $\bar{Q} = 1$ ; then if inputs are  $S = 0$  and  $R = 0$ ,  $G_1$  inputs are a 0 ( $S$ ) and a 1 ( $\bar{Q}$ ). So, its output  $Q = 1$ .  $G_2$  inputs are a 0 ( $R$ ) and a 1 ( $Q$ ) and so its output  $\bar{Q} = 1$ . That is, whatever may be the initial state, when the inputs are  $S = 0$  and  $R = 0$ , both  $Q$  and  $\bar{Q}$  will be equal to 1.

# SR LATCH

 

Case 1 :  $S=0$  ,  $R=0$

Invalid State

$(Q = 1, Q^- = 1)$

Case 2 :  $S=0$ ,  $R=1$

$(Q = 1, Q^- = 0)$

Set State

Case 3:  $S=1$  ,  $R=0$

$(Q = 0 \ Q^- = 1)$

Reset State

Case 4:  $S=1$  ,  $R=1$

Memory State

A	B	A <b>NAND</b> B
0	0	1
0	1	1
1	0	1
1	1	0



## MODULE 4 (TOPIC-3)

# SR FLIPFLOP

[https://youtu.be/23C2FGN\\_wts](https://youtu.be/23C2FGN_wts)




YOUTUBE : SHASTRA TECHNICAL INSTITUTE

# FLIPFLOP CIRCUITS

- Flip flops are actually an application of logic gates. With the help of Boolean logic you can create memory with them.
- Flip flops can also be considered as the most basic idea of a Random Access Memory [RAM]. When a certain input value is given to them, they will be remembered and executed, if the logic gates are designed correctly.
- A higher application of flip flops is helpful in designing better electronic circuits.
- The most commonly used application of flip flops is in the implementation of a feedback circuit. As a memory relies on the feedback concept, flip flops can be used to design it.
 
# SR FLIPFLOP

- In the SR Latch we have seen that output changes occurs immediately after the input changes occurs
- I.e., the latch is sensitive to its S and R inputs at all times
- However it can easily be modified to create a latch that is sensitive to these inputs only when a clock input is active Such a circuit is called SR Flipflop



S	R	Q <sub>N+1</sub>	STATE
0	0	Q <sub>N</sub>	MEMORY
0	1	0	RESET
1	0	1	SET
1	1	X	INVALID

# SR FLIPFLOP

S	R	Q <sub>N+1</sub>	STATE
0	0	Q <sub>N</sub>	MEMORY
0	1	0	RESET
1	0	1	SET
1	1	X	INVALID

**Case 1 :** If  $S = R = 0$  and the clock pulse is applied, the output do not change, i.e.  $Q_{n+1} = Q_n$ . This is indicated in the first row of the truth table.

**Case 2 :** If  $S = 0, R = 1$  and the clock pulse is applied,  $Q_{n+1} = 0$ . This is indicated in the second row of the truth table.

**Case 3 :** If  $S = 1, R = 0$  and the clock pulse is applied,  $Q_{n+1} = 1$ . This is indicated in the third row of the truth table.

**Case 4 :** If  $S = R = 1$  and the clock pulse is applied, the state of the flip-flop is undefined and therefore is indicated as indeterminate in the fourth row of the truth table.

## MODULE 4 (TOPIC-4)

# D FLIPFLOP


<https://youtu.be/tyV1RLUSsAM>




YOUTUBE : SHASTRA TECHNICAL INSTITUTE
 
# D FF

- The basic building block of D Flipflop is SR Flipflop
- The SR FF has two inputs S and R. The S Input is made high to store 1 in the flipflop and R input made high to store 0 in the flipflop
- Looking at the truth table of SR Flipflop we can realize that when both inputs are same the output either does not change or its invalid
- In many practical applications, these inputs are not required
- These inputs conditions can be avoided by making them complement of each other. This modified SR Flipflop is known as **D Flipflop**



# D FF

 


## Case 1 : D=0

Here Output  $Q_{N+1}$  Will be 0, the condition is called **Reset State**
 
## Case 2 : D=1

Here Output  $Q_{N+1}$  Will be 1, the condition is called **Set State**



D	QN+1	STATE
0	0	RESET
1	1	SET

## MODULE 4 (TOPIC-5)

# JK FLIPFLOP

<https://youtu.be/zuH42Y7dH3M>




YOUTUBE : SHASTRA TECHNICAL INSTITUTE



# JK FLIPFLOP

- The unnecessary in the state of SR Flipflop When  $S=1, R=1$  can be eliminated by converting it into JK Flipflop.
- The data input are J and K which are ANDed with  $Q^-$  and  $Q$  respectively, to obtain S and R inputs . Thus

$$S = J Q^-$$
$$R = K Q$$

 

# JK FLIPFLOP

## Case 1 : $J = K = 0$

When  $J = K = 0$ ,  $S = R = 0$  and according to truth table of SR flip-flop there is no change in the output.

When inputs  $J = K = 0$ , output does not change.

## Case 2 : $J = 1$ and $K = 0$

$Q = 0, \bar{Q} = 1$  : When  $J = 1$ ,  $K = 0$  and  $Q = 0$ ,  $S = 1$  and  $R = 0$ . According to truth table of SR flip-flop it is **set** state and the output  $Q$  will be 1.

$Q = 1, \bar{Q} = 0$  : When  $J = 1$ ,  $K = 0$  and  $Q = 1$ ,  $S = 0$  and  $R = 0$ . Since  $SR = 00$ , there is no change in the output and therefore,  $Q = 1$  and  $\bar{Q} = 0$ .

The inputs  $J = 1$  and  $K = 0$ , makes  $Q = 1$ , i.e. **set** state.

## Case 3 : $J = 0$ and $K = 1$

$Q = 0, \bar{Q} = 1$  : When  $J = 0$ ,  $K = 1$  and  $Q = 0$ ,  $S = 0$  and  $R = 0$ . Since  $SR = 00$ , there is no change in the output and therefore,  $Q = 0$  and  $\bar{Q} = 1$ .

$Q = 1, \bar{Q} = 0$  : When  $J = 0$ ,  $K = 1$  and  $Q = 1$ ,  $S = 0$  and  $R = 1$ . According to truth table of SR flip-flop it is a **reset** state and the output  $Q$  will be 0.

The inputs  $J = 0$  and  $K = 1$ , makes  $Q = 0$ , i.e., **reset** state.

## Case 4 : $J = K = 1$


$Q = 0, \bar{Q} = 1$  : When  $J = K = 1$  and  $Q = 0$ ,  $S = 1$  and  $R = 0$ . According to truth table of SR flip-flop it is a **set** state and the output  $Q$  will be 1.

$Q = 1, \bar{Q} = 0$  : When  $J = K = 1$  and  $Q = 1$ ,  $S = 0$  and  $R = 1$ . According to truth table of SR flip-flop it is a **reset** state and the output  $Q$  will be 0.

The input  $J = K = 1$ , toggles the flip-flop output.

J	K	QN+1	STATE
0	0	QN	MEMORY
0	1	0	RESET
1	0	1	SET
1	1	QN BAR	TOGGLE

# JK FLIPFLOP

 

J	K	Q <sub>N+1</sub>	STATE
0	0	Q <sub>N</sub>	MEMORY
0	1	0	RESET
1	0	1	SET
1	1	Q <sub>N</sub> BAR	TOGGLE

## MODULE 4 (TOPIC-6)

# T FLIPFLOP


<https://youtu.be/zuH42Y7dH3M>



YOUTUBE : SHASTRA TECHNICAL INSTITUTE
 
# T FLIPFLOP


- T Flipflop is also known as **Toggle Flipflop**. The T Flipflop is the modification of JK Flipflop
- The T Flipflop is obtained from JK Flipflop by connecting both inputs J and K together
- When  $T=0$ ,  $J=K=0$ , hence there is no change in the output
- When  $T=1$ ,  $J=K=1$ , and hence output Toggles


 
# T FLIPFLOP

When  $T=0$ ,  $J=K=0$ , hence there is no change in the output

When  $T=1$ ,  $J=K=1$ , and hence output Toggles



T	QN+1	STATE
0	QN	MEMORY
1	QN BAR	TOGGLE

## MODULE 4 (TOPIC-7)

# RACE AROUND CONDITION AND MASTER SLAVE JK FLIPFLOP


<https://youtu.be/cRjDzE11Pk4>



YOUTUBE : SHASTRA TECHNICAL INSTITUTE

 
# What is Race Around Condition

- For JK Flipflop, When  $J=1$  and  $K=1$ , clock is too long then the state of FF keeps on Toggle which leads to uncertainty in determining the output state of flipflop
- This Problem is called Race Around Condition






 
# Methods of Eliminating Race Around Condition



 $T/2 < \text{Propagation Delay}$   
( Half Time Period is less than Propagation Delay)



Use of Negative Edge  
Triggering

 


Master Slave JK  
Flipflop

# MASTER SLAVE JK FLIPFLOP


- It Consist of Clocked JK Flipflop as master and Clocked JK Flipflop as slave
- Output of the master FF is fed as an input of slave Flipflop
- Clock is connected directly to master flipflop, but it is connected through inverter to slave flipflop
- In the master slave JK Flipflop the State change occurs when flipflop goes through both positive transition of clock and negative transition of the clock. Thus **race around condition** does not exist in master slave JK Flipflop
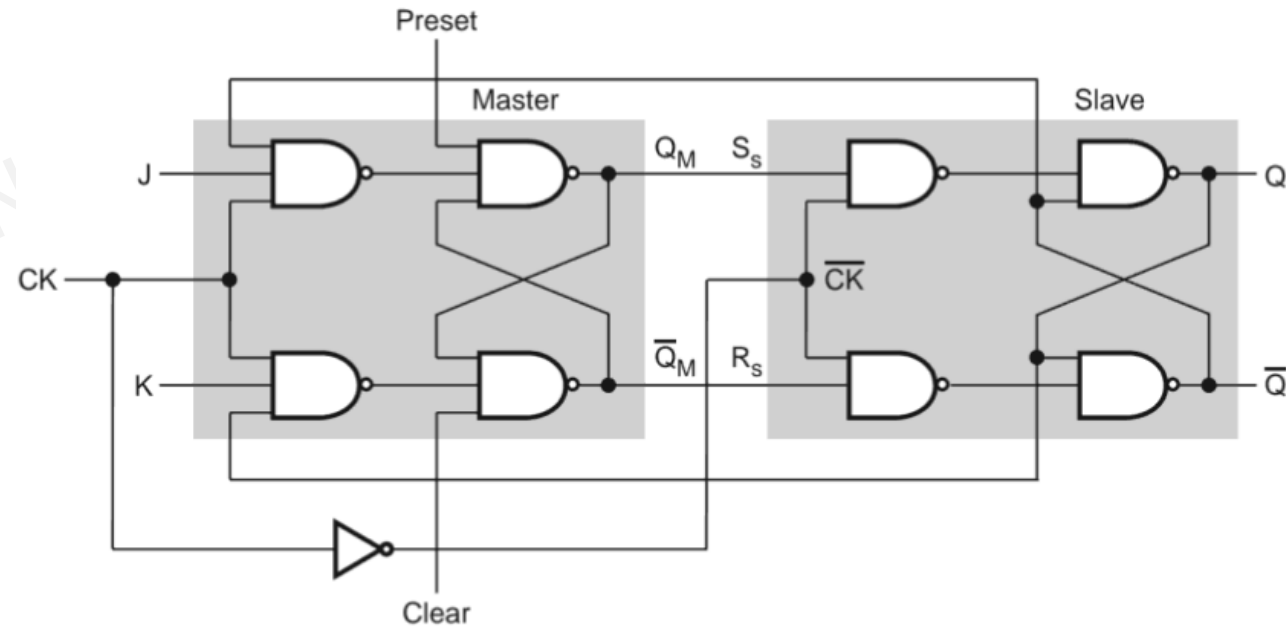
# MASTER SLAVE JK FLIPFLOP

- Figure shows master slave JK Flipflop. Positive clock pulses are applied to first flipflop and inverted clock pulses are applied to second flipflop
- When  $CLK=1$  first FF is enabled, the second flipflop is inhibited because of its clock is low
- When  $CLK=0$ , first FF is Inhibited and Second FF is enabled
- Since the Second flipflop follows first one, it is referred as **slave** and the first one is called **Master**



# MASTER SLAVE JK FLIPFLOP

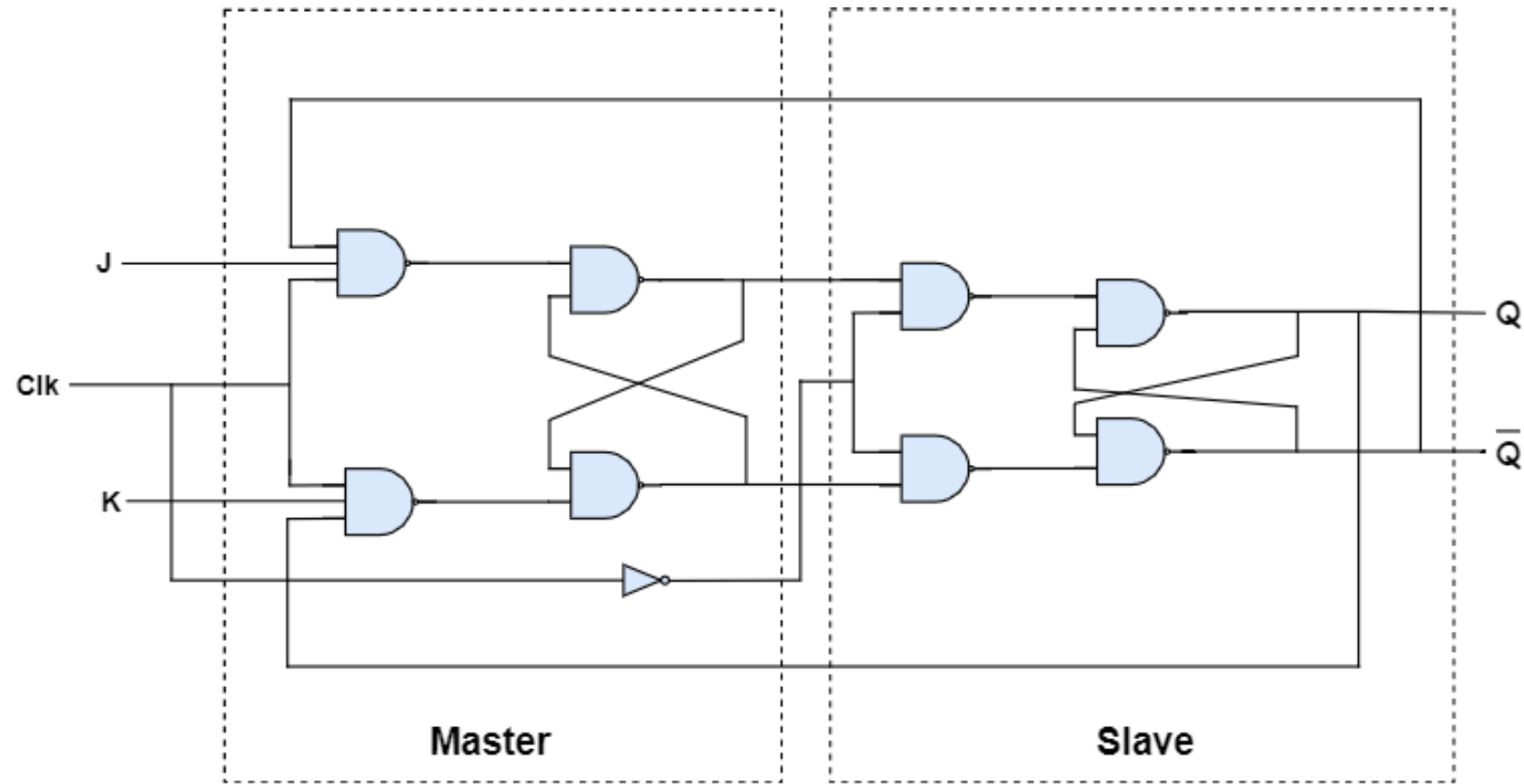

YOUTUBE : SHASTRA TECHNICAL INSTITUTE

## MODULE 3 (TOPIC-8)

# TRUTH TABLE , CHARACTERISTIC TABLE, EXCITATION TABLE CHARACTERISTIC EQUATION OF FLIPFLOP

<https://youtu.be/nDnfLDjOxv0>

YOUTUBE : SHASTRA TECHNICAL INSTITUTE



# SR FLIPFLOP

1 TRUTH TABLE

S	R	QN+1
0	0	QN
0	1	0
1	0	1
1	1	INVALID

3 EXCITATION

On	Qn+1	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

2

CHARACTERISTIC TABLE

QN	S	Q	QN+1
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	X
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	X

# D FLIPFLOP

1

TRUTH TABLE	
D	Q <sub>N+1</sub>
0	0
1	1

2

CHARACTERITIC TABLE		
Q <sub>n</sub>	D	Q <sub>n+1</sub>
0	0	0
0	1	1
1	0	0
1	1	1

3

EXCITATION TABLE		
Q <sub>n</sub>	Q <sub>N+1</sub>	T
0	0	0
0	1	1
1	0	1
1	1	0

# JK FLIPFLOP

1

## TRUTH TABLE

J	K	QN+1
0	0	QN
0	1	0
1	0	1
1	1	QN BAR

3

## EXCITATION

On	Qn+1	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

2

## CHARACTERISTIC TABLE

QN	J	K	QN+1
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0



# T FLIPFLOP

1

TRUTH TABLE	
T	Q <sub>n+1</sub>
0	Q <sub>n</sub>
1	Q <sub>n</sub> bar

2

CHARACTERITIC TABLE		
Q <sub>n</sub>	T	Q <sub>n+1</sub>
0	0	0
0	1	1
1	0	1
1	1	0


3

EXCITATION TABLE		
Q <sub>n</sub>	Q <sub>n+1</sub>	T
0	0	0
0	1	1
1	0	1
1	1	0


# STATE DIAGRAMS




(a) SR flip-flop

 

(b) D flip-flop

 

(c) JK flip-flop

 

(d) T flip-flop

## MODULE 4 (TOPIC-9)

# INTRODUCTION TO COUNTERS

<https://youtu.be/LP4844Om570>

YOUTUBE : SHASTRA TECHNICAL INSTITUTE



# COUNTERS

- Counter is a sequential circuit. A digital circuit which is used for a counting pulses is known counter. Counter is the widest application of flip-flops. It is a group of flip-flops with a clock signal applied. Counters are of two types.

ASYNCHRONOUS COUNTER  
/ RIPPLE COUNTER

SYNCHRONOUS COUNTER

# Synchronous vs Asynchronous Counter

Synchronous Counter	Asynchronous Counter
In synchronous counter, all flip flops are triggered with same clock simultaneously.	In asynchronous counter, different flip flops are triggered with different clock, not simultaneously.
Synchronous Counter is faster than asynchronous counter in operation.	Asynchronous Counter is slower than synchronous counter in operation.
Synchronous Counter does not produce any decoding errors.	Asynchronous Counter produces decoding error.
Synchronous Counter is also called Parallel Counter.	Asynchronous Counter is also called Serial Counter.
Synchronous Counter designing as well implementation are complex due to increasing the number of states.	Asynchronous Counter designing as well as implementation is very easy.
Synchronous Counter will operate in any desired count sequence.	Asynchronous Counter will operate only in fixed count sequence (UP/DOWN).
In synchronous counter, propagation delay is less.	In asynchronous counter, there is high propagation delay.

## MODULE 4 (TOPIC-10)

# ASYNCHRONOUS UP AND DOWN COUNTER

<https://youtu.be/LP4844Om570>

YOUTUBE : SHASTRA TECHNICAL INSTITUTE



# Asynchronous counter

- If the flip-flops do not receive the same clock signal, then that counter is called as **Asynchronous counter**. The output of system clock is applied as clock signal only to first flip-flop. The remaining flip-flops receive the clock signal from output of its previous stage flip-flop. Hence, the outputs of all flip-flops do not change




Up  
Counter

Down  
Counter

Modulo  
Counter

 
# 3 Bit Asynchronous Up Counter

- It Consist of 3 JK Flipflops.
- In order to achieve **Toggle condition**, all the inputs are connected to logical high input ( $J=1$ ,  $K=1$ )
- The initial clock is applied to first flipflop directly. The clock is **negative edge triggered** in order to eliminate race around condition
- The output of 1<sup>st</sup> flipflop is connected to Clock of 2<sup>nd</sup> flipflop
- The output of 2<sup>nd</sup> Flipflop is act as clock of 3<sup>rd</sup> flipflop and so on.





# Timing Diagram and Truth table

 


CLOCK	QC	QB	QA
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

# Asynchronous Down Counter

- The Down Counter will count downwards from a maximum count to zero
- In 4 bit asynchronous down counter, the clock signal is connected to clock of first flipflop
- The clock of remaining flipflop is triggered by QA bar output of previous stage


# 4 Bit Asynchronous Down Counter

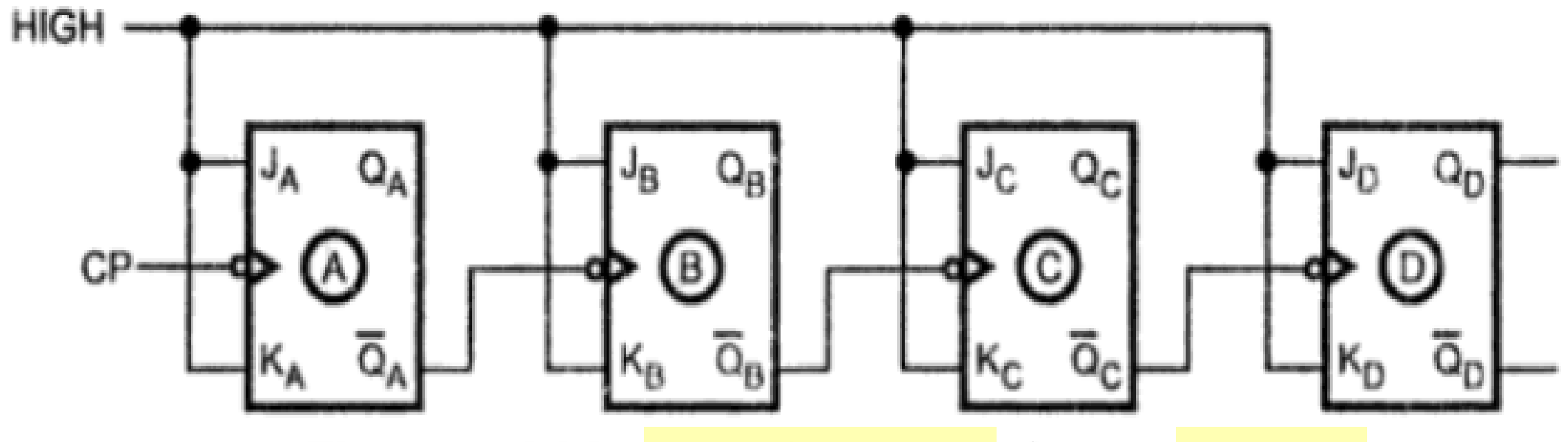

# Asynchronous Down Counter

- The Down Counter will count downwards from a maximum count to zero
- In 4 bit asynchronous down counter, the clock signal is connected to clock of first flipflop
- The clock of remaining flipflop is triggered by QA bar output of previous stage

# Timing Diagram and Truth table

 

CLOCK	QD	QC	QB	QA
0	1	1	1	1
1	1	1	1	0
2	1	1	0	1
3	1	1	0	0
4	1	0	1	1
5	1	0	1	0
6	1	0	0	1
7	1	0	0	0
8	0	1	1	1
9	0	1	1	0
10	0	1	0	1
11	0	1	0	0
12	0	0	1	1
13	0	0	1	0
14	0	0	0	1
15	0	0	0	0

## MODULE 4 (TOPIC-11)

# MODULO COUNTER


<https://youtu.be/LP4844Om570>

YOUTUBE : SHASTRA TECHNICAL INSTITUTE


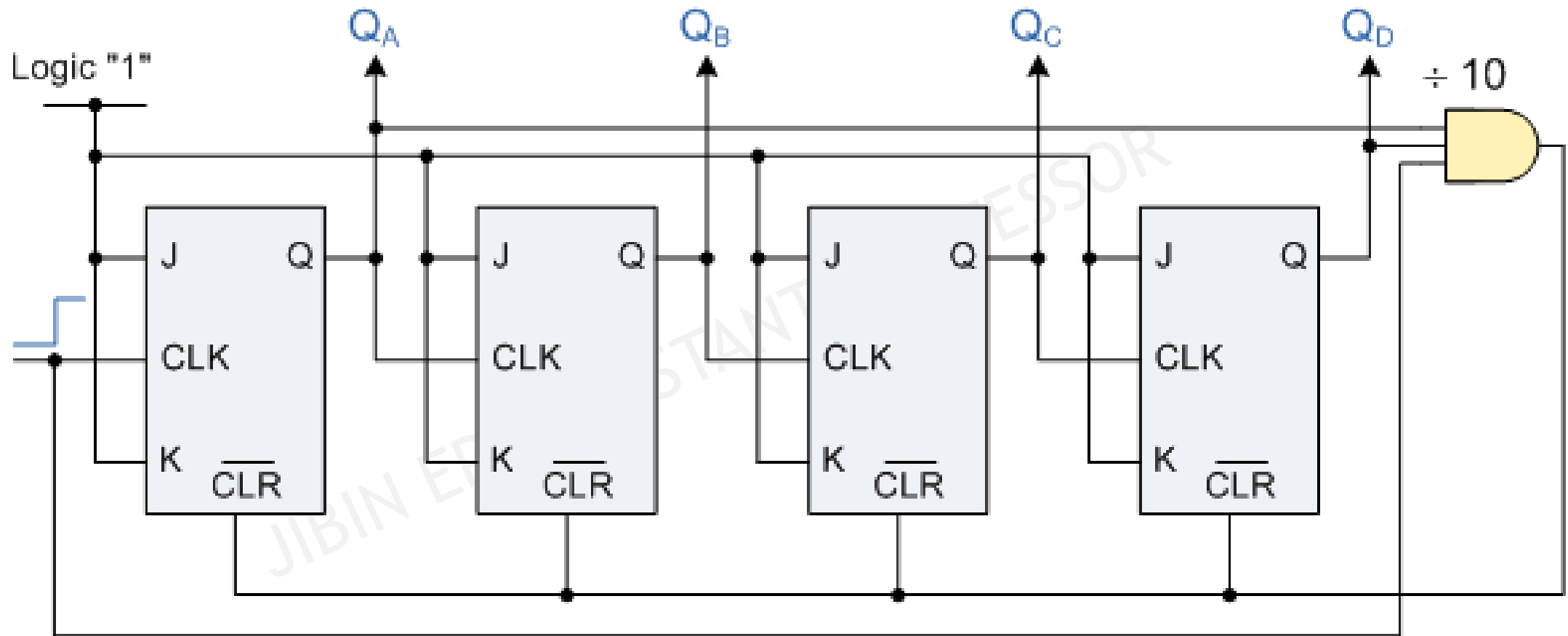
# Asynchronous Decade Counter

- This type of asynchronous counter counts upwards on each leading edge of the input clock signal starting from "0000" until it reaches an output "1010" (decimal 10). Both outputs QB and QD are now equal to logic "1" and the output from the NAND gate changes state from logic "1" to a logic "0" level and whose output is also connected to the CLEAR (CLR) inputs of all the J-K Flip-flops. This causes all of the Q outputs to be reset back to binary "0000" on the count of 10. Once QB and QD are both equal to logic "0" the output of the NAND gate returns back to a logic level "1" and the counter restarts again from "0000". We now have a decade or Modulo-10 counter




YOUTUBE : SHASTRA TECHNICAL INSTITUTE



**Decade Counter Truth Table**

Clock Count	Output bit Pattern				Decimal Value
	QD	QC	QB	QA	
1	0	0	0	0	0
2	0	0	0	1	1
3	0	0	1	0	2
4	0	0	1	1	3
5	0	1	0	0	4
6	0	1	0	1	5
7	0	1	1	0	6
8	0	1	1	1	7
9	1	0	0	0	8
10	1	0	0	1	9
11	Counter Resets its Outputs back to Zero				

## Decade Counter Timing Diagram

 


YOUTUBE : SHASTRA TECHNICAL INSTITUTE

# MODULO-10 COUNTER (BCD Counter)


- A good example of a modulo-m counter circuit which uses external combinational circuits to produce a counter with a modulus of 10 is the Decade Counter. Decade (divide-by-10) counters such as the TTL 74LS90, have 10 states in its counting sequence making it suitable for human interfacing where a digital display is required.
- The decade counter has four outputs producing a 4-bit binary number and by using external AND and OR gates we can detect the occurrence of the 9th counting state to reset the counter back to zero. As with other mod counters, it receives an input clock pulse, one by one, and counts up from 0 to 9 repeatedly.
- Once it reaches the count 9 (1001 in binary), the counter goes back to 0000 instead of continuing on to 1010. The basic circuit of a decade counter can be made from JK flip-flops that switch state on the negative trailing-edge of the clock signal as shown.

# MODULO-10 COUNTER (BCD Counter)

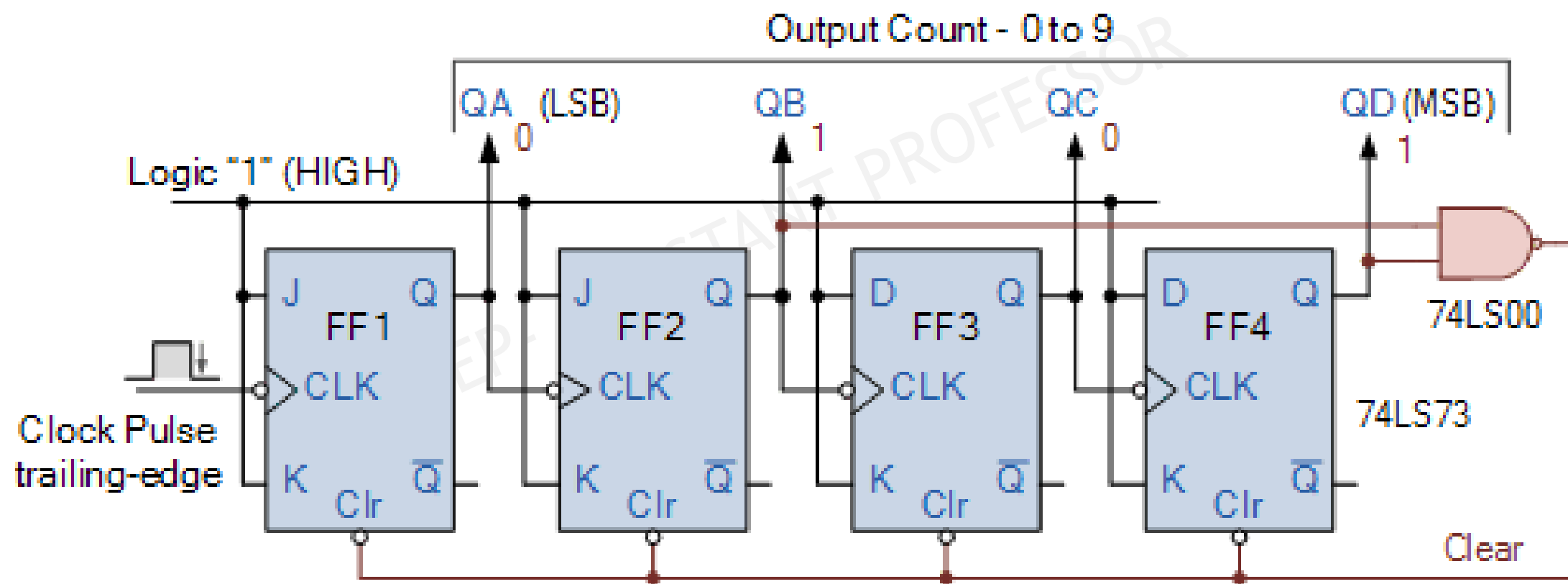

## MODULE 4 (TOPIC-12)

# SYNCHRONOUS COUNTER

<https://youtu.be/PF39iLI1r4g>  
<https://youtu.be/pPMXScXy0ZE>  **YouTube**


YOUTUBE : SHASTRA TE

# Steps to design synchronous counter

Decide the number of flipflops



Excitation table of Flipflop



State diagram and circuit excitation table




Obtain simplified equation using kmap



Draw the logic diagram

# Synchronous Counter

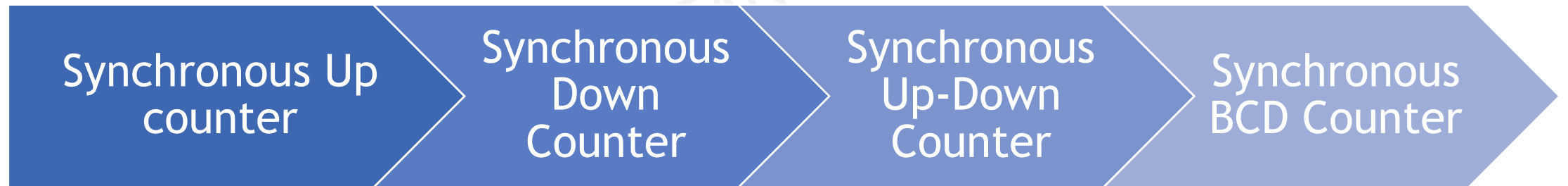

JK Excitation Table			
$Q_n$	$Q_{n+1}$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

T Excitation Table		
$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0



# 1- Design Mod-5 Synchronous Counter using JK Flipflop

**Step 1 :** Determine the number of flip-flop needed

Flip-flops required are

$$2^n \geq N$$

Here  $N = 5 \quad \therefore \quad n = 3$  i.e. three flip-flops are required.

**Step 2 :** Type of flip-flop to be used : JK

**Step 3 :** Determine the excitation table for the counter.

$Q_n$	$Q_{n+1}$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

**Table 4.6.1 Excitation table for JK flip-flop**

# 1- Design Mod-5 Synchronous Counter using JK Flipflop

Present State			Next State			Flip-flop Inputs					
$Q_C$	$Q_B$	$Q_A$	$Q_{C+1}$	$Q_{B+1}$	$Q_{A+1}$	$J_C$	$K_C$	$J_B$	$K_B$	$J_A$	$K_A$
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	0	0	0	X	1	0	X	0	X
1	0	1	X	X	X	X	X	X	X	X	X
1	1	0	X	X	X	X	X	X	X	X	X
1	1	1	X	X	X	X	X	X	X	X	X

Table 4.6.2 Excitation table for counter

# 1- Design Mod-5 Synchronous Counter using JK Flipflop

## Step 4 : K-Map simplification

**For  $J_C$**

$Q_B Q_A$	00	01	11	10
0	0	0	1	0
1	X	X	X	X

$$J_C = Q_B Q_A$$

**For  $K_C$**

$Q_B Q_A$	00	01	11	10
0	X	X	X	X
1	1	X	X	X

$$K_C = 1$$

**For  $J_B$**

$Q_B Q_A$	00	01	11	10
0	0	1	X	X
1	0	X	X	X

$$J_B = Q_A$$

**For  $K_B$**

$Q_B Q_A$	00	01	11	10
0	X	X	1	0
1	X	X	X	X

$$K_B = Q_A$$

**For  $J_A$**

$Q_B Q_A$	00	01	11	10
0	1	X	X	1
1	0	X	X	X

$$J_A = \bar{Q}_C$$


**For  $K_A$**

$Q_B Q_A$	00	01	11	10
0	X	1	1	X
1	X	X	X	X

$$K_A = 1$$

# 1- Design Mod-5 Synchronous Counter using JK Flipflop

**Step 5 :** Draw the logic diagram

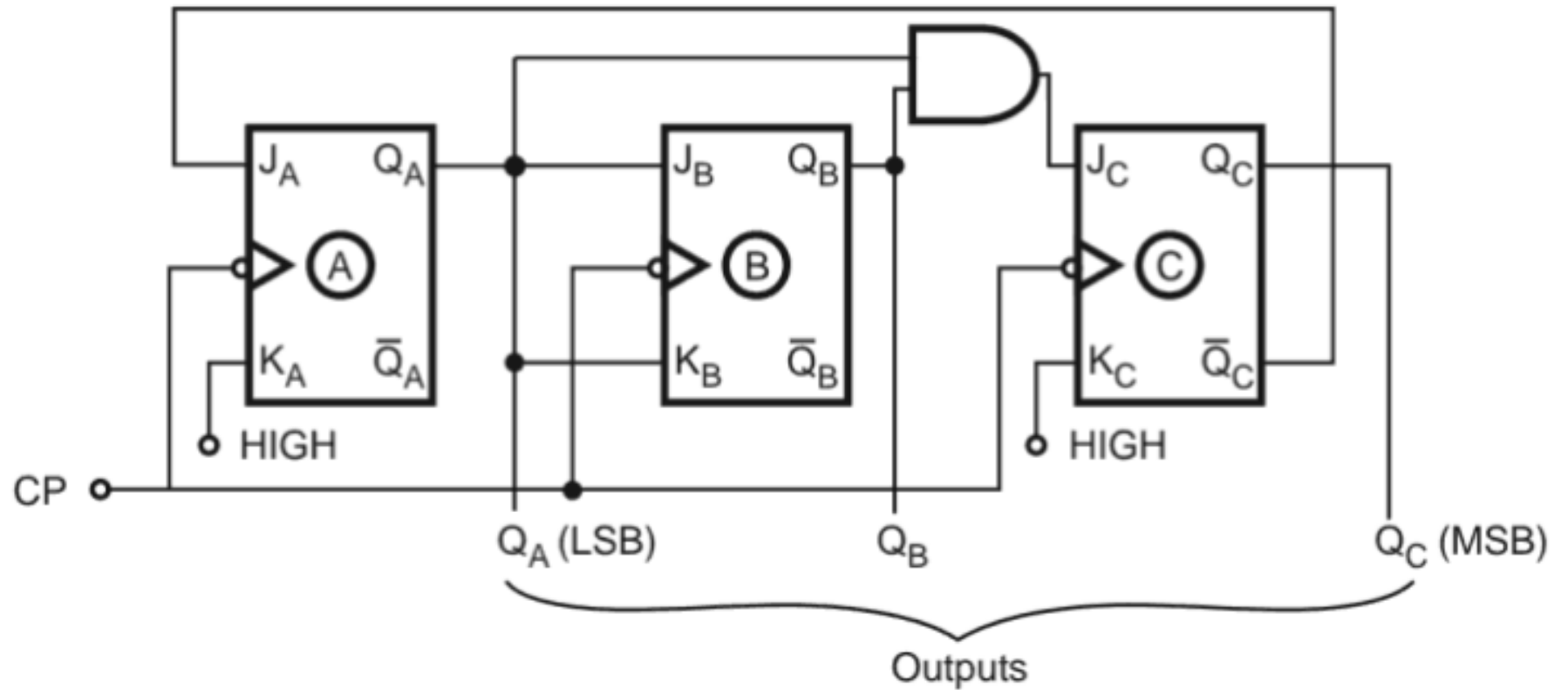

2- Using Positive Triggering SR Flipflop design a counter counts in the following sequence 000,111,110,101,100,011,010,001,000....

**Step 1 :** Determine the number of flip-flops needed

We know that  $2^n \geq N$ . Here,  $N = 8 \quad \therefore n = 3$

**Step 2 :** Type of flip-flop to be used : SR

## 2- Using Positive Triggering SR Flipflop design a counter counts in the following sequence 000,111,110,101,100,011,010,001,000....

**Step 3 :** Determine the excitation table for counter.

Here, the next state for each present state is written according to given sequence. For example, the next state for the present state 000 is 111.

$Q_n$	$Q_{n+1}$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

Table 4.6.5 Excitation table of SR flip-flop

Present state			Next state			Flip-flop inputs					
A	B	C	$A^+$	$B^+$	$C^+$	$S_A$	$R_A$	$S_B$	$R_B$	$S_C$	$R_C$
0	0	0	1	1	1	1	0	1	0	1	0
0	0	1	0	0	0	0	x	0	x	0	1
0	1	0	0	0	1	0	x	0	1	1	0
0	1	1	0	1	0	0	x	x	0	0	1
1	0	0	0	1	1	0	1	1	0	1	0
1	0	1	1	0	0	x	0	0	x	0	1
1	1	0	1	0	1	x	0	0	1	1	0
1	1	1	1	1	0	x	0	x	0	0	1

Table 4.6.6 Excitation table for counter

## 2- Using Positive Triggering SR Flipflop design a counter counts in the following sequence 000,111,110,101,100,011,010,001,000....

**Step 4 : K-map simplification.**

**For  $S_A$**

BC \ A	00	01	11	10
0	1	0	0	0
1	0	X	X	X

$$S_A = \bar{A} \bar{B} \bar{C}$$

**For  $R_A$**

BC \ A	00	01	11	10
0	0	X	X	X
1	1	0	0	0

$$R_A = A \bar{B} \bar{C}$$

**For  $S_B$**

BC \ A	00	01	11	10
0	1	0	X	0
1	1	0	X	0

$$S_B = \bar{B} \bar{C}$$

**For  $R_B$**

BC \ A	00	01	11	10
0	0	X	0	1
1	0	X	0	1

$$R_B = B \bar{C}$$

**For  $S_C$**

BC \ A	00	01	11	10
0	1	0	0	1
1	1	0	0	1

$$S_C = \bar{C}$$


**For  $R_C$**

BC \ A	00	01	11	10
0	0	1	1	0
1	0	1	1	0

$$R_C = C$$

2- Using Positive Triggering SR Flipflop design a counter counts in the following sequence 000,111,110,101,100,011,010,001,000....

**Step 5 :** Draw logic diagram

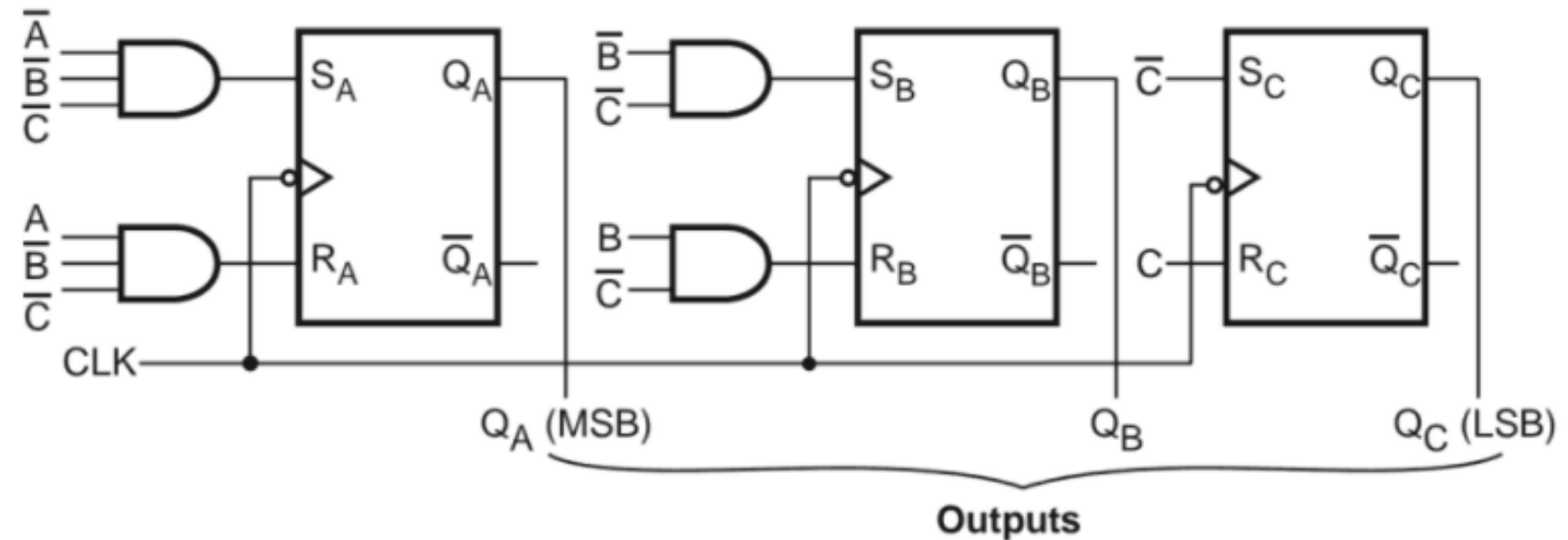

**Fig. 4.6.5 (b) Logic diagram**



2- Using Positive Triggering SR Flipflop design a counter counts in the following sequence 000,111,110,101,100,011,010,001,000....

JIBIN EP- ASSISTANT PROFESSOR

YOUTUBE : SHASTRA TECHNICAL INSTITUTE

### 3- Design 3 Bit Synchronous UP-Down Counter using T Flipflop

#### **Step 1 : Determine Number of Flipflops**

It require 3 T Flipflops


### 3- Design 3 Bit Synchronous UP-Down Counter using T Flipflop

#### Step 2 : The Excitation Table

T Excitation Table		
$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0

### 3- Design 3 Bit Synchronous UP-Down Counter using JK Flipflop

#### Step 3 : Draw the State Diagram

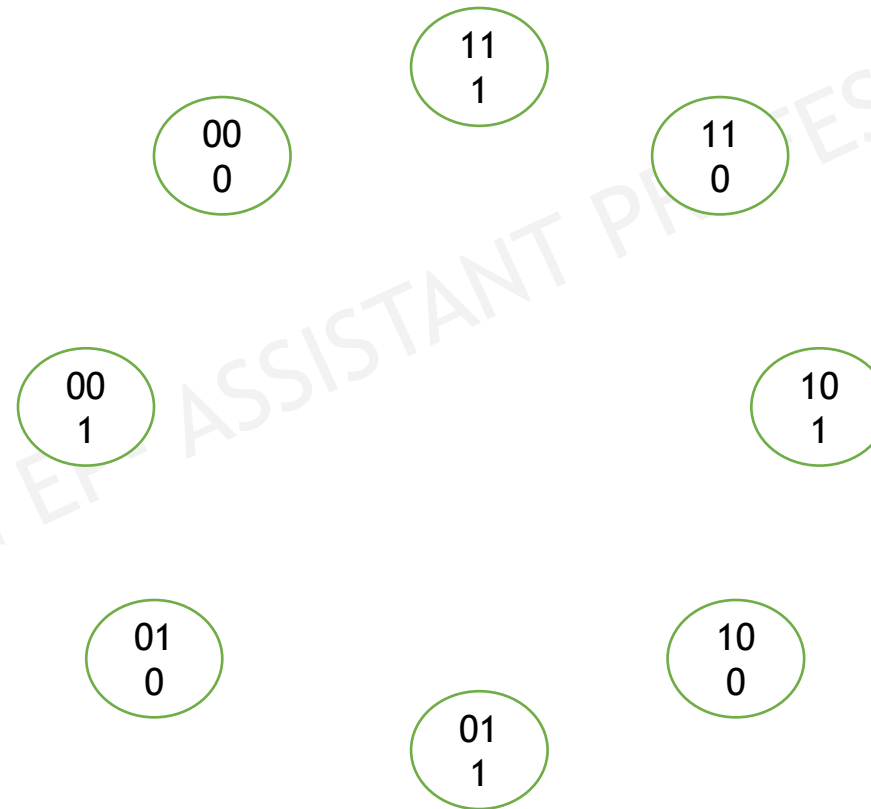

**$M=0$**   
**UPCOUNTER**

**$M=1$**   
**DOWN COUNTER**

### 3- Design 3 Bit Synchronous UP-Down Counter using T Flipflop

#### Step 3B : The Circuit Excitation Table

Mode	Present State			Next State			Required Excitation		
	Q2	Q1	Q0	Q2*	Q1*	Q0*	T2	T1	T0
0	0	0	0	0	0	1	0	0	1
0	0	0	1	0	1	0	0	1	1
0	0	1	0	0	1	1	0	0	1
0	0	1	1	1	0	0	1	1	1
0	1	0	0	1	0	1	0	0	1
0	1	0	1	1	1	0	0	1	1
0	1	1	0	1	1	1	0	0	1
0	1	1	1	0	0	0	1	1	1
1	0	0	0	1	1	1	1	1	1
1	0	0	1	0	0	0	0	0	1
1	0	1	0	0	0	1	0	1	1
1	0	1	1	0	1	0	0	0	1
1	1	0	0	0	1	1	1	1	1
1	1	0	1	1	0	0	0	0	1
1	1	1	0	1	0	1	0	1	1
1	1	1	1	1	1	0	0	0	1

T Excitation Table		
Qn	Qn+1	T
0	0	0
0	1	1
1	0	1
1	1	0

# Design 3 Bit Asynchronous UP-Down Counter using T Flipflop

**K Map Simplification and Logic Diagram**  
**(Kindly Workout)**

JIBIN EP- ASSISTANT PROFESSOR

**PREPARED BY**



Jibin EP

**SHAstra  
TECHNICAL  
INSTITUTE**

KTU | PSC | UPSC



**Jibin EP**

Assistant Professor

Department of Electronics and Communication  
Eranad Knowledge City Technical Campus Manjeri

Contact : 9633908979, 70121716607

Email : [epjibin@gmail.com](mailto:epjibin@gmail.com), [jibin@ekc.edu.in](mailto:jibin@ekc.edu.in)



<https://www.youtube.com/ShastraTechnicalInstitute>