

# Digital System Design

## Module 4 - SEQUENTIAL LOGIC CIRCUITS

Dr. Deepthi Sasidharan

Assistant Professor, Department of Information Technology  
GEC Barton Hill, Thiruvananthapuram

November 4, 2020


# ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS

- ▶ The behavior of a clocked sequential circuit is determined from the inputs, the outputs, and the state of its flip-flops.
- ▶ The outputs and the next state are both a function of the inputs and the present state.
- ▶ The analysis of a sequential circuit consists of obtaining a table or a diagram for the time sequence of inputs, outputs, and internal states.
- ▶ It is also possible to write Boolean expressions that describe the behavior of the sequential circuit.

# State Equations

A *state equation* (also called a *transition equation*) specifies the next state as a function of the present state and inputs.

# Analyse the Circuit

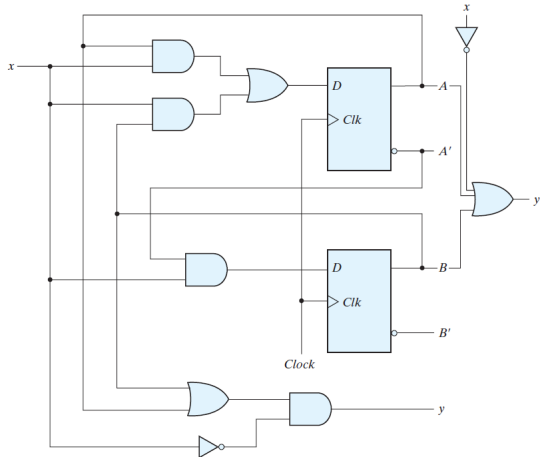

# State Table

Present State		Input	Next State		Output
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0