

Digital System Design


Module 4 - SEQUENTIAL LOGIC CIRCUITS

Dr. Deepthi Sasidharan

Assistant Professor, Department of Information Technology
GEC Barton Hill, Thiruvananthapuram

November 2, 2020

D Latch (Transparent Latch)



 


(a) Logic diagram


En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

(b) Function table

Graphic symbols for latches

   


Clock response in latch and flip-flop

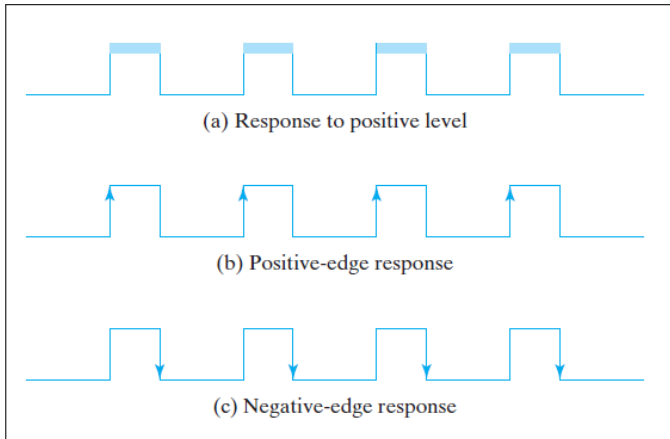

Flip-Flops


- ▶ There are two ways that a latch can be modified to form a flip-flop.
 1. Employ two latches in a special configuration that isolates the output of the flip-flop and prevents it from being affected while the input to the flip-flop is changing.
 2. Trigger only during a signal transition (from 0 to 1 or from 1 to 0) of the synchronizing signal (clock) and is disabled during the rest of the clock pulse

Master-slave D flip-flop

 


- ▶ Edge-Triggered D Flip-Flop

 
D -type positive-edge-triggered flip-flop



 Graphic symbol for edge-triggered D flip-flop



(a) Positive-edge

 

(a) Negative-edge