

Reg No.:

Name:

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
 Third Semester B.Tech Degree Examination December 2021 (2019 scheme)

Course Code: ITT203

Course Name: DIGITAL SYSTEM DESIGN

Max Marks: 100

Duration: 3 Hours

PART A*Answer all questions. Each question carries 3 marks*

Marks

- 1 Convert (94.75)₁₀ to binary, octal and hexadecimal. (3)
- 2 Explain about Excess-3 code & Gray code. (3)
- 3 State duality principle. Find the dual of the Boolean expression (3)

$$F(A,B,C) = (A+B'C)(A+C)$$
- 4 Realize the X-OR function using NOR logic. (3)
- 5 Implement the function $F = \sum m(0, 2, 3, 5)$ using 8 to 1 Mux. (3)
- 6 Design an even parity generator circuit for transmitting four bits of information. (3)
- 7 Derive the characteristic table and characteristics equations of D, JK and T flip-flops. (3)
- 8 Draw the circuit implementation of a positive edge triggered D flip-flop. (3)
- 9 What is the difference between a register and a counter? Give examples that clearly shows the difference between them. (3)
- 10 Explain a Ring Counter. Draw the timing diagram of a 4-bit Ring Counter for 8 clock pulses. Assuming that the counter was initialized with 0110 at time $T=0$. (3)

PART B*Answer any one full question from each module. Each question carries 14 marks***Module 1**

- 11 a) Perform subtraction using 1's & 2's complement method. (8)
 i) $11010 - 10111$
 ii) $100 - 11000$
 b) Represent the decimal numbers 453.8 and 628.6 in BCD. Calculate the sum using BCD arithmetic. (6)
- 12 Express the signed decimal numbers (+12) and (-7) using 2's complement. (14)

representation and enough digits to accommodate the numbers. Then perform the binary multiplication on them.

Module 2

- 13 a) Simplify the Boolean function $F(A, B, C, D) = \sum m(0, 1, 2, 5, 8, 9, 10)$ into: (8)
- sum-of-products form and
 - product-of-sums form:

- b) Expand $A + BC' + ABD' + ABCD$ to minterms and maxterms (6)

- 14 a) Simplify the following functions using Quine- McClusky method (8)

$$F(v, w, x, y, z) = \sum m(0, 1, 6, 7, 8, 9, 13, 14, 15)$$

- b) Find all the prime implicants for the Boolean function (6)

$$F(w, x, y, z) = \sum (0, 1, 2, 5, 7, 8, 10, 15)$$

Also, determine the essential prime implicants. Give the simplified Boolean expression

Module 3

- 15 a) Explain a 4-bit carry look ahead adder with neat diagram (7)
- b) Design a 4-bit code-converter to convert BCD to gray code (7)
- 16 Design a four-bit combinational circuit 2's complementer (The output generates the 2's complement of the input binary number) Implement the circuit using basic gates (14)

Module 4

- 17 a) Explain the working of D flip-flop with preset and clear input (8)
- b) What you mean by asynchronous inputs and synchronous inputs in flip flop (6)
- 18 a) A synchronous sequential machine has a single control input X and the clock, and outputs A & B. On consecutive rising edges of the clock, the code on A and B changes from 00 to 01 to 10 to 11 and repeats itself if X=1, if at any time, X=0, it holds to the present state. Draw the state diagram and implement the circuit using T flip flop (10)
- b) Differentiate between edge triggering and level triggering of flip flops. Give an example of edge triggered and level triggered circuit (4)

Module 5

- 19 Show the difference between a synchronous counter and an asynchronous counter using the design of a BCD counter (14)
- 20 a) Explain a four-bit universal shift register (7)
- b) Design a combinational circuit using a ROM. The circuit accepts a three-bit number and outputs a binary number equal to the square of the input number. (7)
