

Ques 1. Tutorials 1-3

1. Convert each of the following decimal numbers to BCD:

$$a. 2439 \quad b. 4091 \quad c. 1475$$

Ans: a.  $(2439)_D = (0010)_{BCD} (0100)_{BCD} (0011)_{BCD} (1001)_{BCD}$

b.  $(4091)_D = (0100)_{BCD} (0000)_{BCD} (1001)_{BCD} (0001)_{BCD}$

c.  $(1475)_D = (0001)_{BCD} (0100)_{BCD} (0111)_{BCD} (0101)_{BCD}$

2. Convert each of the following BCD codes to decimal.

$$a. 1000\ 0110 \quad b. 0011\ 0101\ 0001 \quad c. 1001\ 0100\ 0110\ 0000$$

Ans: a.  $(1000, 0110)_{BCD} = (86)_{10}$

b.  $(0011, 0101, 0001)_{BCD} = (351)_{10}$

c.  $1001\ 0100\ 0110\ 0000 = (9470)_{10}$

3. Add the following BCD numbers

$$a. 0011 + 0100 \quad c. 10010100 + 10010111$$

$$b. 00100011 + 00010101 \quad d. 01100111 + 01010011$$

Ans: a)  $\begin{array}{r} 0011 \\ + 0100 \\ \hline 0111 \end{array}$

b)  $\begin{array}{r} 0010 \\ 0010 \\ + 0001 \\ \hline 0011 \end{array}$

c)  $\begin{array}{r} 1001\ 0110 \\ + 1001\ 0111 \\ \hline 10010110 \end{array}$

d)  $\begin{array}{r} 0110\ 0111 \\ + 0101\ 0011 \\ \hline 1100\ 1010 \end{array}$

4. How does an exclusive-OR gate differ from an OR gate in its logical operation?

Ans: XOR

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

\* Output is 'true' if either of the inputs are 'true'.  
The output is 'false' if both inputs are 'false'.  
Or if both inputs are true.

5. Determine the sequence of ASCII codes required for writing your roll number, Name is in the following format and also express it in hexadecimal.

Ans:  $\langle 47, \langle \text{NITHIN} \rangle$

ASCII - 60556244606582671265786562

Hex - 3C373E2C3C41524348414E41

6. For the Boolean functions

$$F = x\bar{y}z + \bar{x}\bar{y}z + \bar{w}x\bar{y} + w\bar{z}cy + wxy$$

- Obtain the truth table of F.
- Draw the logic diagram, using the original Boolean expressions.
- Use Boolean algebra to simplify the functions to a minimum number of literals.
- Obtain the truth table of the functions from the simplified expressions and show that it is the same as the one in part(a).
- Draw the logic diagram from the simplified expressions, and compare

8. Using boolean algebra, simplify the following expressions

a)  $A\bar{B} + A\bar{B}C + A\bar{B}C\bar{D} + A\bar{B}CDE$

$\text{Ans } AB \cdot AB \cdot I$

$$= AB \cdot (C + \bar{C}) = AB \cdot C + AB \cdot \bar{C} = A\bar{B}C(D + \bar{D})$$

$$= A\bar{B}CD + A\bar{B}C\bar{D} + AB\bar{C}D + ABC\bar{D}$$

$$= A\bar{B}CD(E + \bar{E}) + A\bar{B}C\bar{D}(E + \bar{E}) + AB\bar{C}D(E + \bar{E}) + ABC\bar{D}\bar{E}$$

$$= A\bar{B}CDE + A\bar{B}C\bar{D}\bar{E} + AB\bar{C}\bar{D}\bar{E} + A\bar{B}\bar{C}DE + A\bar{B}\bar{C}\bar{D}\bar{E} + A\bar{B}\bar{C}\bar{D}\bar{E}$$

$\equiv$

$$\Rightarrow A\bar{B}C = A\bar{B}C \cdot I = A\bar{B}C(D + \bar{D}) = A\bar{B}C(D + A\bar{B}C\bar{D})$$

$$= A\bar{B}CD(E + \bar{E}) + A\bar{B}C\bar{D}(E + \bar{E})$$

$$= A\bar{B}CDE + A\bar{B}C\bar{D}\bar{E} + AB\bar{C}\bar{D}\bar{E} + A\bar{B}\bar{C}DE$$

$$\Rightarrow A\bar{B}CD = A\bar{B}CD \cdot I = A\bar{B}CD(E + \bar{E}') = A\bar{B}CDE + A\bar{B}C\bar{D}\bar{E}'$$

$$= A\bar{B}CDE + A\bar{B}CD\bar{E}$$

$$\therefore A\bar{B} + A\bar{B}C + A\bar{B}CD + A\bar{B}CDE$$

$$= \underline{A\bar{B}CDE} + A\bar{B}CD\bar{E} + A\bar{B}CDE + A\bar{B}C\bar{D}\bar{E} + A\bar{B}CDE +$$

$$A\bar{B}CDE + A\bar{B}C\bar{D}\bar{E} + A\bar{B}CDE + A\bar{B}C\bar{D}\bar{E} + A\bar{B}CDE +$$

$$AB\bar{D}\bar{E} + A\bar{B}\bar{D}\bar{E} + A\bar{B}CDE + A\bar{B}C\bar{D}\bar{E} + A\bar{B}CDE + A\bar{B}C\bar{D}\bar{E} +$$



26/10/22 Tutorial 30.10.22 (36/3) A

Q Simplify the following boolean functions

$$1) F(x,y,z) = \sum_m(2,3,6,7)$$

$$2) F(A,B,C,D) = \sum_m(0,1,2,3,8,10,12)$$

$$3) F(w,x,y,z) = \sum_m(3,7,11,13,14,15)$$

$$4) F = x'z + w'yz + w(x'y + xy)$$

$$5) F = wxyt + xz + w(z + w)x(t + A) = ?$$

$$\text{Ans: } 1) F(x,y,z) = \sum_m(2,3,6,7)$$

	$x^2$	$y^2$	$z^2$	$w^2$	$xz$	$yz$	$wz$	$wx$	$wy$	$xy$	$wxy$
$x^1$	0	1	0	0	0	0	0	0	0	0	0
$x^1$	1	0	1	0	0	0	0	0	0	0	0
$x^1$	0	1	1	0	0	0	0	0	0	0	0
$x^1$	1	1	0	0	1	0	0	0	0	0	0
$y^1$	0	0	0	0	0	0	0	0	0	0	0
$y^1$	1	0	0	0	0	0	0	0	0	0	0
$y^1$	0	1	0	0	0	0	0	0	0	0	0
$y^1$	1	1	0	0	1	0	0	0	0	0	0
$z^1$	0	0	0	0	0	0	0	0	0	0	0
$z^1$	1	0	0	0	0	0	0	0	0	0	0
$z^1$	0	1	0	0	0	0	0	0	0	0	0
$z^1$	1	1	0	0	1	0	0	0	0	0	0
$w^1$	0	0	0	0	0	0	0	0	0	0	0
$w^1$	1	0	0	0	0	0	0	0	0	0	0
$w^1$	0	1	0	0	0	0	0	0	0	0	0
$w^1$	1	1	0	0	1	0	0	0	0	0	0

$$F = A'B + A'C'D + ABCD$$

AB	C'D	C'D	CD	CD
AB'	0	1	1	2
A'B	4	5	7	6
AB	12	13	15	14
AB'	6	7	11	10

$$3) F(w,x,y,z) = \sum_m(3,7,11,13,14,15)$$

$wz$	$y^2$	$z^2$	$yz$	$z^2$	$wz$	$w^2$	$wy$	$wz$	$w^2$	$wy$	$wxy$
0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0	0	0	0
0	1	1	1	1	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

$$F = y^2 + wz + wy$$

$$4) F = x'z + wxy + w(x'y + zy)$$


$wx$	$y^2$	$z^2$	$yz$	$z^2$	$wx$	$w^2$	$wy$	$wx$	$w^2$	$wy$	$wxy$
0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0	0	0	0
0	1	1	1	1	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

$$F = xy + z^2 + wz$$

$$5) F = wxy + xz + wxz^2 + wz$$

$wx$	$y^2$	$z^2$	$wz$	$w^2$	$wx$	$w^2$	$wy$	$wx$	$w^2$	$wy$	$wxy$
0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0	0	0	0
0	1	1	1	1	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

$$F = wz + wy$$

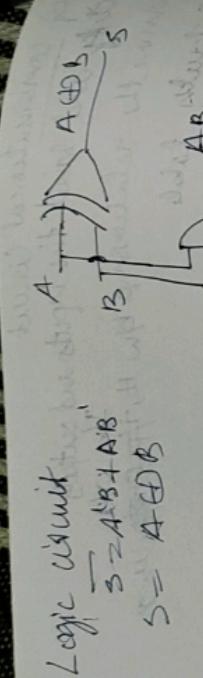

#### Tutorial 4

\* Use the k-map method to implement the minimum expression for the logic function specified in given truth table.

AB	c'd'	c'd	cd'	cd
A'B'	0	0	1	1
A'B	0	0	1	1
AB	1	1	0	0
AB'	1	0	0	1

\* Find all the prime implicants for the following Boolean function, and determine which are essential.

d)  $F(AB, CD) = \sum(0, 2, 3, 5, 7, 8, 10, 11, 14, 15)$

AB	c'd'	c'd	cd'	cd
A'B'	1	0	1	1
A'B	0	1	0	1
AB	0	0	1	1
AB'	1	0	0	1

Prime implicants =  $B'D$ ,  $A'BD + CD + AC$ ,  
essential =  $BD$ ,  $AB + CD$

$$F = B'D + A'BD + CD + AC$$

b)  $F(W, X, Y, Z) = \sum(1, 3, 6, 7, 8, 9, 12, 13, 14, 15)$

W	X	Y	Z	WZ	YZ	YZ'	Y'Z
W	0	0	0	0	0	0	1
W	0	0	1	0	0	1	0
W	0	1	0	0	0	0	0
W	0	1	1	0	1	1	0
W	1	0	0	0	0	0	0
W	1	0	1	0	0	0	0
W	1	1	0	0	1	0	0
W	1	1	1	1	1	0	0

$$F = WY + XY + X'Z$$

prime implicants =  $WY$ ,  $XY$ ,  $X'Z$   
essential components =  $XY$ ,  $X'Z$

Prime implicants =  $WY$ ,  $XY$ ,  $X'Z$   
essential components =  $XY$ ,  $X'Z$

\* Draw a NAND logic diagram that complements the complement of the following function. Also, draw its logic diagram only using NOR gates.

$$F(A,B,C,D) = \sum(0,1,2,3,6,10,11,14)$$

$$AB \vee CD \vee C'D' \vee CD' \quad F = ABC + A'B'C + C'D'$$


AB	CD	C'D'	CD'	F
1 1	1 1	0 0	1 1	1
1 1	0 0	1 1	0 0	1
0 0	1 1	0 0	1 1	1

(AB = draw prime)

AB	CD	C'D'	CD'	F
1 1	0 0	1 1	0 0	1
1 1	1 1	0 0	1 1	1
0 0	0 0	1 1	0 0	1

(AB = draw prime)
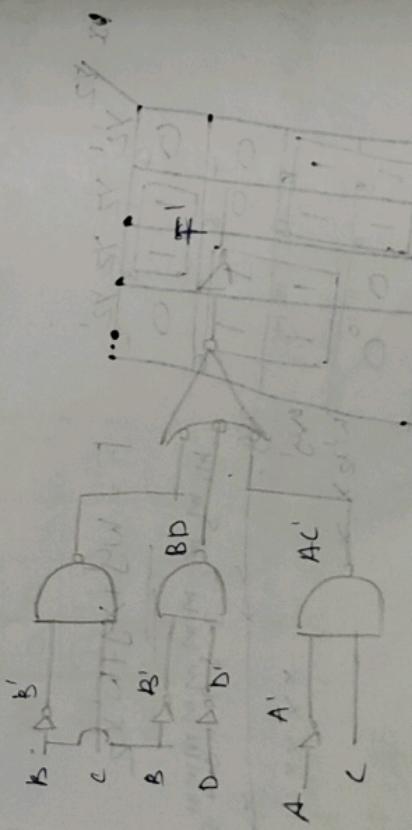
$$F = BC + BD + AC + A'D + C'D + (A'D + C'D)' + (BC + BD)'$$



$$\begin{aligned} F &= A'B'D + A'BC + A'B'C'D + B'C'D'E + A'D'E + A'B'C'D' \\ &\underline{\underline{ABCD + ABC'D}} \end{aligned}$$


It can be reduced to a single term  
using Boolean algebra laws

14 0 1110  
 15 0 1111  
 16 10000  
 17 10001  
 18 10010  
 19 10011

### Tutorial - 5

### Module 3

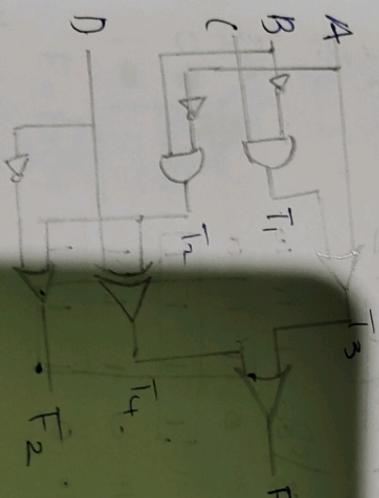1. Consider the combinational circuit shown in figure below



Truth table

- b) List the truth table with 16 binary combinations of the four input variables. Then list the binary values for  $\bar{T}_1$ , through  $\bar{T}_4$  and outputs  $F_1$  and  $F_2$  in the table.
- c) Plot the output Boolean functions obtained in part (b) on maps and show that the simplified Boolean expressions are equivalent to those obtained in part (a).

- d) Derive the Boolean expressions for  $T_1$  through  $T_4$ . Evaluate the outputs  $F_1$  and  $F_2$  as a function of the four inputs.

Ans 2)  $T_1 = \bar{B}C$ ,  $T_2 = A'B$   
 $T_3 = A+B'C$ ,  $T_4 = A'BCD$   
 $= (A'B'D + A'BD') + A'BD$   
 $= AD + A'B + A'BD'$

$F_1 = T_3 + T_4$   
 $= A'B'C + A'D + B'D + A'BD'$   
 $= A(I+D) + B'C + B'D + A'BD'$   
 $= (\cancel{AB}D') + B'C + B'D$   
 $= (A+A')(CA + BD') + B'C + BD$   
 $= A + BD + B'C + BD$

$F_2 = T_5 = A'B + D$

b)  $ABCD \quad T_1 \quad T_2 \quad T_3 \quad T_4 \quad F_1 \quad F_2$   
 $\begin{array}{cccccc} 0000 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0001 & 0 & 0 & 0 & 1 & 1 & 1 \\ 0010 & 1 & 0 & 1 & 0 & 1 & 0 \\ 0011 & 1 & 0 & 1 & 1 & 1 & 1 \\ 0100 & 0 & 1 & 0 & 0 & 1 & 1 \\ 0101 & 0 & 1 & 0 & 1 & 0 & 1 \\ 0110 & 0 & 1 & 1 & 0 & 0 & 1 \\ 0111 & 0 & 1 & 1 & 1 & 1 & 1 \end{array}$   
 $F_2 = D + A'B$

$ABCD \quad T_1 \quad T_2 \quad T_3 \quad T_4 \quad F_1$   
 $\begin{array}{cccccc} 1 & 1 & 0 & 0 & 0 & 1 \\ 1 & 1 & 0 & 1 & 0 & 0 \\ 1 & 1 & 1 & 0 & 0 & 1 \\ 1 & 1 & 1 & 1 & 0 & 0 \end{array}$

K-map for $F_1$					
A	B	00	01	11	10
00	0	1	1	1	0
01	1	0	0	1	1
11	1	1	1	1	1
10	1	1	1	1	1

$F_1 = ABD' + B'D + B'C$

K-map for  $F_2$

K-map for $F_2$					
A	B	00	01	11	10
00	0	1	1	0	1
01	1	1	1	1	1
11	0	1	1	1	1
10	0	1	1	1	1

$F_2 = D + A'B$


2) Design a combinational circuit with 3 inputs and one output. The output is 1 when the binary value of the input is less than 3. The output is 0 otherwise.

K-map for $F$										
x	y	z	000	001	010	011	100	101	110	111
0	0	0	1	1	1	1	0	0	0	0
0	0	1	1	1	1	1	0	0	0	0
0	1	0	1	1	1	1	0	0	0	0
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	0	0	0	1	1	1	1
1	0	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	1	1	1	1
1	1	1	0	0	0	0	1	1	1	1

3) Design a combinational circuit with 3 inputs and one output. The output is 1 when the binary value of the input is an even number.


K-map for $F$										
x	y	z	000	001	010	011	100	101	110	111
0	0	0	1	1	1	1	0	0	0	0
0	0	1	1	1	1	1	0	0	0	0
0	1	0	1	1	1	1	0	0	0	0
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	0	0	0	1	1	1	1
1	0	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	1	1	1	1
1	1	1	0	0	0	0	1	1	1	1

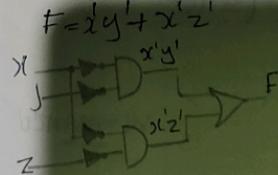4) Design a combinational circuit with three inputs  $x, y$  and  $z$  and three outputs  $A, B$  and  $C$ . When the binary input is 9, 10 or 11 the binary output is one greater than the input. When the binary input is 4, 5, 6 or 7 the binary output is two less than the input.



Ans x y z A B C

0 0 0	0 1 0
0 0 1	0 1 1
0 1 0	1 0 0
0 1 1	1 0 1
1 0 0	0 1 0
1 0 1	0 1 1
1 1 0	1 0 0
1 1 1	1 0 1

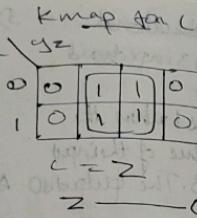

5. Design a code converter that converts a decimal digit from the 8, 4, -2, +1 code to BCD.

Kmap for A

x y z	0 0 0 1 1 1 0
0 0 0	1 1 1
1 0 0	1 1 1

$$A = y$$

y — A

Kmap for B

x y z	0 0 0 1 1 1 0
0 1 1	0 0 0
1 1 1	0 0 0

$$B = y'$$

y — B

Ans:

Decimal digit	8 4 -2 +1	BCD (8+2)
A B C D	W x g <sub>2</sub>	
0 0 0 0	0 0 0 0	0 0 0 0
0 1 1 1	0 1 1 1	0 0 0 0
1 0 1 0	0 1 1 0	0 0 1 0
1 1 0 1	0 1 0 1	0 1 0 1
0 0 1 1	0 1 0 0	0 1 0 1
0 1 0 1	1 0 1 1	0 1 0 0
1 0 0 1	1 0 1 0	0 1 1 0
1 1 1 0	1 0 0 1	0 1 1 1

Map for W

x y z	0 0 0 1 1 1 0
0 0 0	0 X X X
0 1 1	0 0 0 0
1 1 1	X X 1 X
1 0 0	1 0 0 0

$$W = AB + AC'D$$

Kmap for L

0	0	1	1	0
1	0	1	1	0

$$L = Z$$

Map for DC

AB CD	0 x x x
0 0	1 0 0 0
0 1	x 0 x x
1 0	0 1 1 1

$$x = BC'D + B'D + BC$$

Map for Y

AB CD	0 1 1 1 1 0
0 0	0 x x x
0 1	0 1 0 1
1 1	x x 0 x
1 0	1 0 0 1

$$y = CD' + C'D = C \oplus D$$


$$Z = D$$


(b) A Majority circuit is a combinational circuit where output is equal to 1 if the input variables have more 1's than 0's the output is 0 otherwise. Design a simple majority circuit of finding 3 inputs truth table, Boolean equations and a logical diagram.

Ans x y z F

0 0 0	0 0 0
0 0 1	0 1 0
0 1 0	0 1 0
0 1 1	1 0 1
1 0 0	1 0 0
1 0 1	1 0 0
1 1 0	1 1 0
1 1 1	1 1 1

$$F = g_2 + xz + yz$$

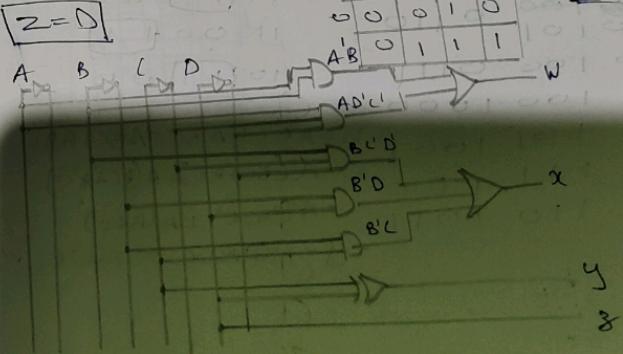

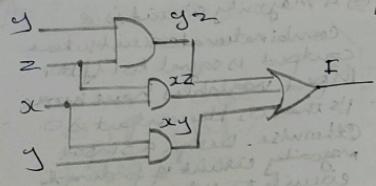

Q1) Design a combinational circuit that converts a 4-bit Gray code to a 4-bit binary no. Implement the circuit with OR-OR gate.

Ans:

Input	Output
A B C D	W Z Y 2
0 0 0 0	0 0 0 0
0 0 0 1	0 0 0 1
0 0 1 0	0 0 1 0
0 0 1 1	0 0 1 1
0 1 0 0	0 1 0 1
0 1 0 1	0 1 1 0
0 1 1 0	0 1 1 1
0 1 1 1	1 0 0 0
1 0 0 0	1 0 0 1
1 0 0 1	1 0 1 0
1 0 1 0	1 0 1 1
1 0 1 1	1 1 0 0
1 1 0 0	1 1 0 1
1 1 0 1	1 1 1 0
1 1 1 0	1 1 1 1

AB \ CD	00	01	10	11
00	0	0	0	0
01	0	1	0	1
10	1	0	1	0
11	1	1	1	1

AB \ CD	00	01	10	11
00	0	0	0	0
01	1	1	1	1
10	0	0	0	0
11	1	1	1	1


$$Z = A'B + AB' = A \oplus B$$

AB \ CD	00	01	11	10
00	0	0	1	0
01	1	1	0	0
11	0	0	1	1
10	1	1	0	0

$$\begin{aligned} Y &= A'B'C + A'B'C' + ABC + ABC' \\ &= A'(BC + BC') + A(B + B'C') \\ &= A'(B(C + C')) + A(B + C') \\ Y &= A \oplus B \oplus C = X \oplus C \end{aligned}$$

AB \ CD	00	01	11	10
00	0	1	1	0
01	1	0	0	1
11	0	0	1	1
10	1	0	0	0
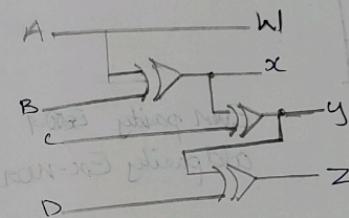
$$\begin{aligned} Z &= A \oplus B \oplus C \oplus D \\ &= Y \oplus D \end{aligned}$$



Magnitude Comparator

B <sub>1</sub> , B <sub>2</sub>	00	01	11	10
A <sub>1</sub> , A <sub>2</sub>	00	01	11	10
00	1	1	1	0
01	1	1	0	1
11	0	0	1	1
10	1	0	0	0

$$L = A_1'B_1 + A_1'A_2B_2 + A_2'B_2$$

29/11/22 Tutorial

IA	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
0	0	0	0	1	0	1	1	0	0	0	0
0	0	0	1	0	1	1	0	1	0	0	1
0	0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	0	1	1	0	0	1	1
0	1	0	1	1	1	0	1	1	0	1	1
0	1	1	0	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0	0
1	0	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1	1

K-map for 'a'

AB	CD	00	01	11	10
00	00	1	0	1	1
01	0	1	1	1	1
11	0	0	0	0	0
10	1	1	0	0	0

$$a = A'C + A'BD + ABC' + B'C'D'$$

K-map for 'b'

AB	CD	00	01	11	10
00	00	1	1	1	1
01	0	1	0	0	0
11	0	0	0	0	0
10	1	1	0	0	0

$$b = A'B' + A'C'D' + A'CD + ABCD$$

K-map for 'c'

AB	CD	00	01	11	10
00	00	1	1	1	0
01	0	1	1	1	1
11	0	0	0	0	0
10	1	1	0	0	0

$$c = A'B + A'D + ABC + B'C'D$$

K-map for 'd'

AB	CD	00	01	11	10
00	00	1	0	1	1
01	0	1	0	0	1
11	0	0	0	0	0
10	1	1	0	0	0

$$d = A'B'C + A'CD + AB'C' + B'C'D + A'B'C'D$$

K-map for 'e'

AB	CD	00	01	11	10
00	00	1	0	0	1
01	0	0	0	0	1
11	0	0	0	0	0
10	1	0	0	0	0

$$e = A'CD' + B'C'D'$$

K-map for  $f'$



AB\CD	00 01	11 10
00	1 0 0 0	0 1 0 0
01	0 1 0 0	0 0 1 0
11	0 0 0 0	0 0 0 0
10	1 1 0 0	0 0 0 0

$$f = A'C'D' + ABC'D + A'BC'D + A'B'D'$$

K-map for  $g$

AB\CD	00 01 11 10
00	0 0 0 1
01	0 1 0 0
11	0 0 0 0
10	1 1 0 0

$$g = AB'C' + A'BC' + A'B'C + A'CD'$$

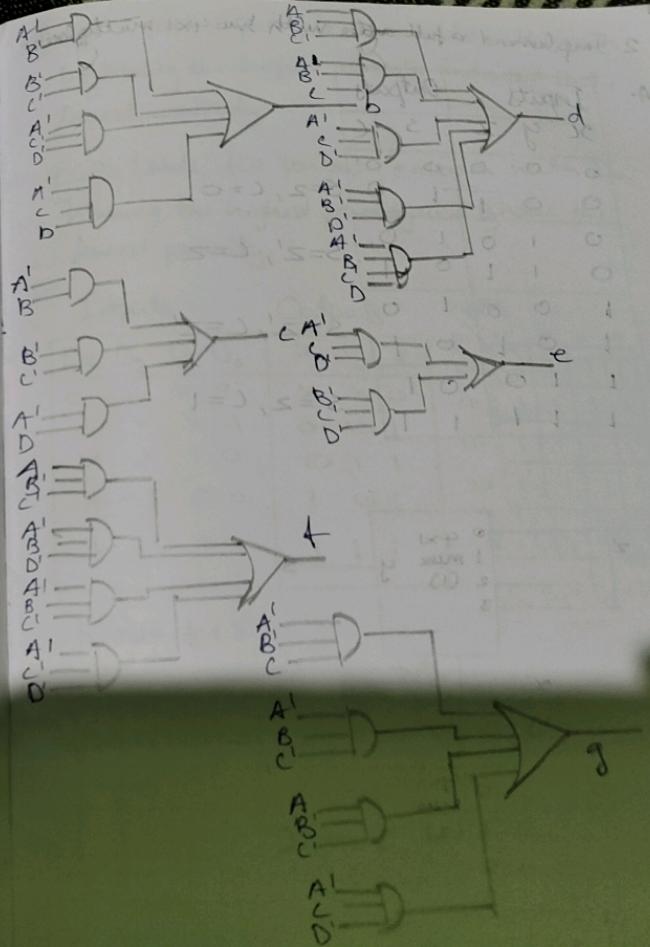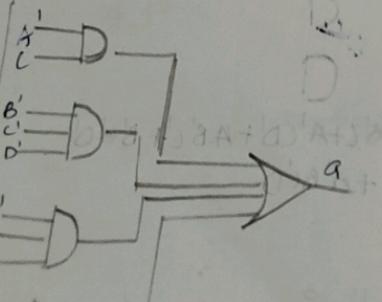

2. Implement a full adder with two 4x1 multiplexers

Inputs	Outputs
x y z	s c
0 0 0	0 0
0 0 1	1 0
0 1 0	1 0
0 1 1	0 1
1 0 0	1 0
1 0 1	0 1
1 1 0	0 1
1 1 1	1 1

Inputs	Outputs
z y x	s c
0 0 0	0 0
0 0 1	1 0
0 1 0	1 0
0 1 1	0 1
1 0 0	1 0
1 0 1	0 1
1 1 0	0 1
1 1 1	1 1



$$S = Z_1, C = 0$$

$$S = Z_1, C = Z$$

$$S \neq Z_1, C = Z$$

Inputs	Outputs
1 1 0	0 1
1 1 1	1 1

$$S = Z_1, C = 1$$

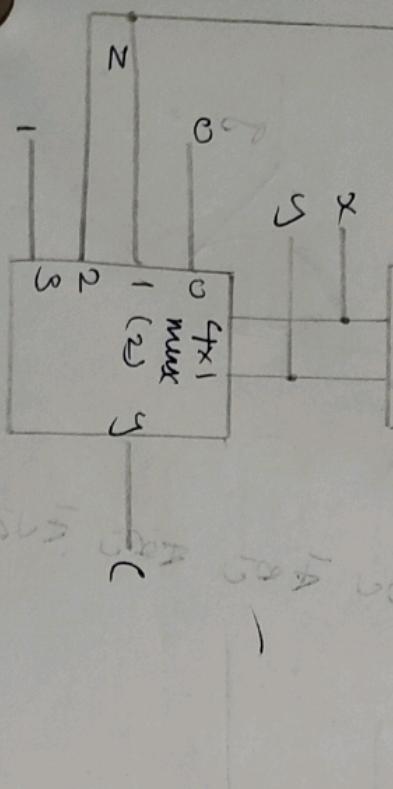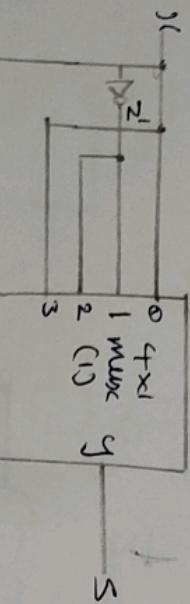

3. Design a four-input priority encoder with input D<sub>0</sub> having the highest priority and input D<sub>3</sub> the lowest priority

A. Truth table for priority encoder with D<sub>0</sub> having the highest priority and D<sub>3</sub> having the lowest priority.

Inputs	Outputs
D <sub>3</sub> D <sub>2</sub> D <sub>1</sub> D <sub>0</sub>	x y v
0 0 0 0	x x 0
0 0 0 1	0 0 1
0 0 1 0	1 0 1
0 0 1 1	1 0 0
0 1 0 0	1 0 1
0 1 0 1	1 0 0
0 1 1 0	1 0 0
1 0 0 0	1 1 1

D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	v
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$N = (D_3, D_2, D_1, D_0)$$

$$N = D_3 + D_2 + D_1 + D_0$$


K map for N

D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	N
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	N
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$N = D_3 + D_2 + D_1 + D_0$$

$$N = D_3' D_2' + D_1' D_0'$$

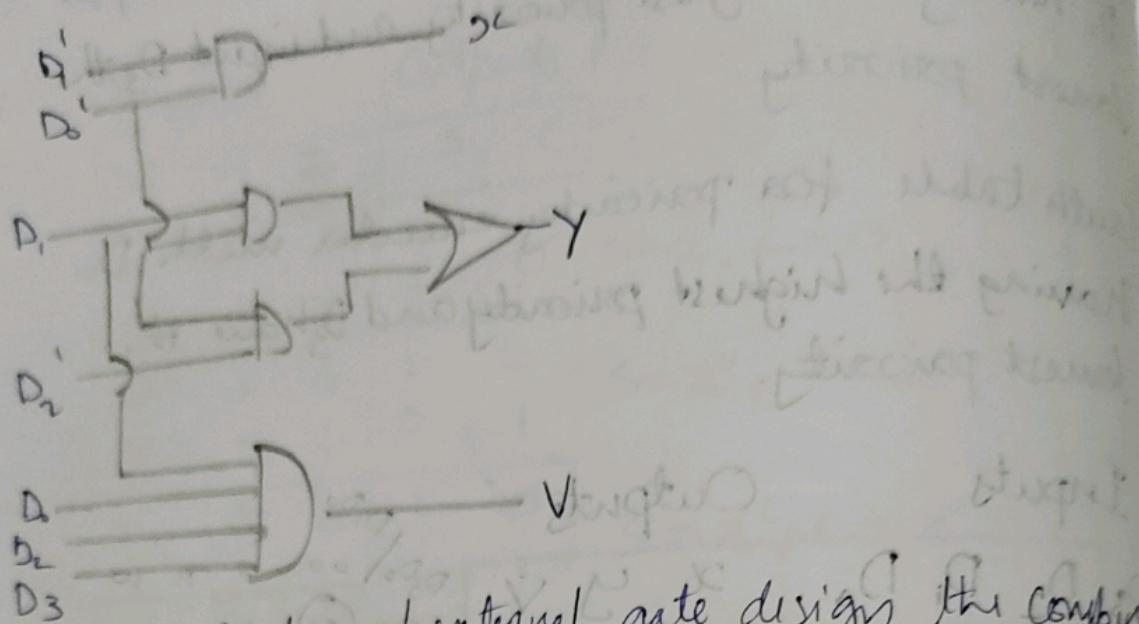


4. Using a decoder and external gate designs the combination circuit defined by the following 3 boolean functions

$$F_1 = x'y'z' + x'z = x'y'z' + xy'z + xyz' = \sum m(2, 5, 7)$$

$$F_2 = x'y'z' + x'y = x'y'z' + (y'z + xy'z) = \sum m(2, 3, 4)$$

$$F_3 = x'y'z' + xz = x'y'z' + xy'z + xyz' = \sum m(0, 6, 7)$$

$x$	$y$	$z$	$F_1$	$F_2$	$F_3$
0	0	0	0	0	1
0	0	1	0	0	0
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	0	1	0
1	0	1	0	1	0
1	1	0	1	0	0
1	1	1	1	0	1

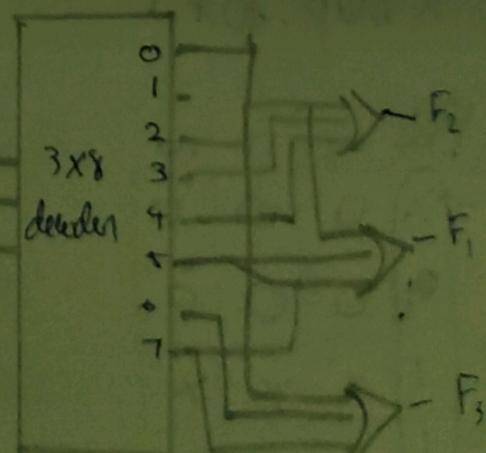

combine  
m  
sequential  
It might  
\*Free  
\*Stack  
\*Time