

Digital System Design

Module 4 - SEQUENTIAL LOGIC CIRCUITS

Dr. Deepthi Sasidharan

Assistant Professor, Department of Information Technology
GEC Barton Hill, Thiruvananthapuram

November 10, 2020

DESIGN PROCEDURE

- ▶ From the word description and specifications of the desired operation, derive a state diagram for the circuit.
- ▶ Reduce the number of states if necessary.
- ▶ Assign binary values to the states.
- ▶ Obtain the binary-coded state table.
- ▶ Choose the type of flip-flops to be used.
- ▶ Derive the simplified flip-flop input equations and output equations.
- ▶ Draw the logic diagram.

State Table

Reducing the State Table


Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>e</i>	<i>f</i>	0	1

Reduced State Table

Reduced State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	d	0	1
e	a	d	0	1

State diagram

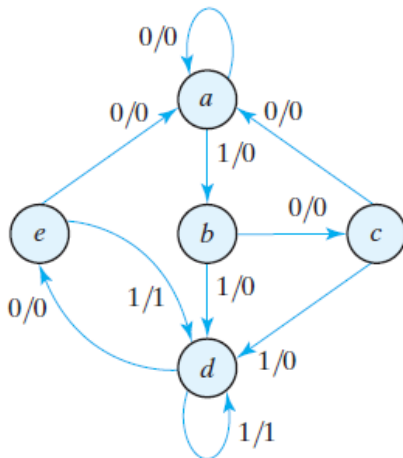

State Assignment

Three Possible Binary State Assignments

State	Assignment 1, Binary	Assignment 2, Gray Code	Assignment 3, One-Hot
a	000	000	00001
b	001	001	00010
c	010	011	00100
d	011	010	01000
e	100	110	10000

State Assignment

Reduced State Table with Binary Assignment 1

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
000	000	001	0	0
001	010	011	0	0
010	000	011	0	0
011	100	011	0	1
100	000	011	0	1